

Code: CS1T5, IT1T5/ IT2T3RS

**I B.Tech - I Semester – Regular/Supplementary Examinations
November 2018**

**BASIC ELECTRICAL ENGINEERING
(Common to CSE & IT)**

Duration: 3 hours

Max. Marks: 70

PART – A

Answer *all* the questions. All questions carry equal marks

11 x 2 = 22 M

1. a) Write statements of Kirchhoff's laws?
- b) Distinguish between ideal and practical voltage source?
- c) Write any two analogies between electric and magnetic circuits?
- d) Explain the dot convention used in magnetically coupled circuits?
- e) Define peak factor?
- f) Define RMS value of sinusoidal waveform with expression?
- g) What is the function of holding coil in a 3-point starter?
- h) Define the slip of an induction motor.
- i) Why rating of the transformer is given in KVA? Explain.
- j) Define controlling and damping torque.
- k) A 100Ω resistance is directly switched on across a 10 V battery. What is the current through resistor? How much is the power loss?

PART – B

Answer any **THREE** questions. All questions carry equal marks.

$$3 \times 16 = 48 \text{ M}$$

2. a) Two batteries E1 and E2 having e.m.fs of 6V and 2V respectively and internal resistances of 2 and 3 ohms are connected in parallel across a 5 ohm resistor. Calculate
i) the current through each battery (ii) terminal voltage

8 M

- b) When three resistors are connected in parallel show the relation between the currents and obtain the equation for currents.

8 M

3. a) Derive the relation between self inductance, mutual inductance and coefficient of coupling.


8 M

- b) What is a magnetic circuit? Compare magnetic circuit with an electric circuit.

8 M

4. a) Calculate the average and rms value for a half -wave rectified sinusoidal quantity as shown in figure.

8 M

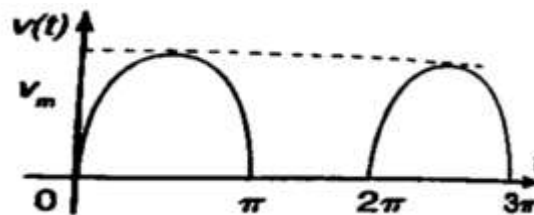

b) A coil has a resistance of 4Ω and an inductance of 9.55 mH . Calculate (i) the reactance, (ii) the impedance, and (iii) the current taken from a 240V , 50 Hz supply. Determine also the phase angle between the supply voltage and current. 8 M

5. a) Explain the working of D.C. motor with neat diagram. 8 M

b) Explain the concept of rotating magnetic field? 8 M

6. a) Explain construction and working of a Single phase transformer? 8 M

b) Describe the working of a moving iron instrument with a neat sketch. 8 M