

Code: EE2T5

**I B.Tech - II Semester – Regular/Supplementary Examinations –
May 2017**

**ELECTRICAL CIRCUIT ANALYSIS - I
(ELECTRICAL & ELECTRONICS ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

PART – A

Answer *all* the questions. All questions carry equal marks

11x 2 = 22 M

1.

- a) Define Link and twig.
- b) What is the difference between an ideal source and a practical source? Draw the relevant characteristics of the above sources.
- c) Determine I_x in the circuit shown in Figure-1 by using nodal analysis

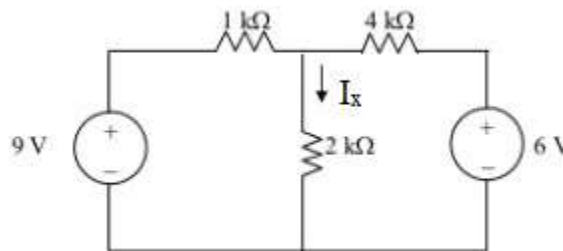


Figure-1

- d) Determine V_o in the circuit shown in Figure-2 by using mesh analysis.

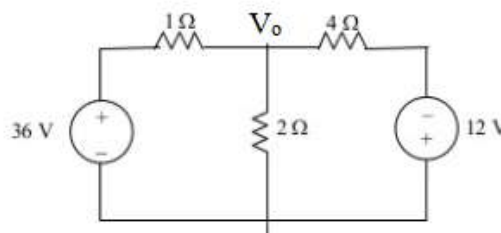


Figure-2

- e) Find the r.m.s value of the voltage wave whose equation is,
 $v(t)=10+200 \sin(\omega t-30^0)+100 \cos 3\omega t -50 \sin (\omega t+60^0)$
- f) Calculate the resistance and inductance or capacitance in series for each of the following impedances. Assume the frequency to be 60Hz. i) $12+j30$ ii) $-j60$
- g) Draw the locus diagram for the impedance in R-C series circuit with XC variable.
- h) Define resonance in electrical circuit and write condition for resonance in RLC series circuit.
- i) Write advantages of three phase system over single phase.
- j) Give the relationship between line and phase voltages in star and delta connected 3-phase system.
- k) Calculate equivalent resistance between P and Q in the circuit shown in Figure-3

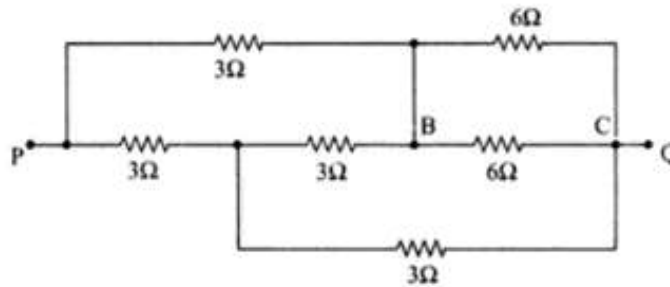


Figure – 3

PART – B

Answer any **THREE** questions. All questions carry equal marks.

3 x 16= 48 M

2. a) The wave form of the current flowing through an inductor of 6 mH is as shown in Figure-4. Determine and sketch waveform of voltage and power. 8 M

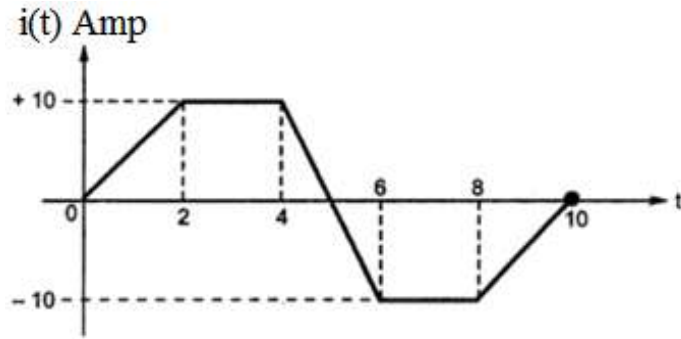


Figure-4

b) Calculate current I supplied by battery in circuit shown in Figure-5. 8 M

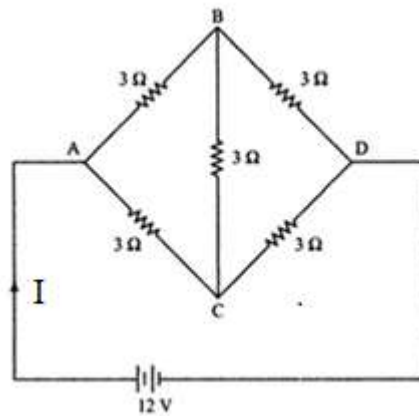


Figure-5

3. a) Find the node voltages in the circuit shown in Figure-6. 8 M

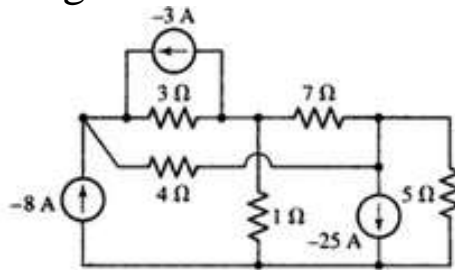


Figure-6

b) Determine current i_1 in the circuit of Figure-7. 8 M

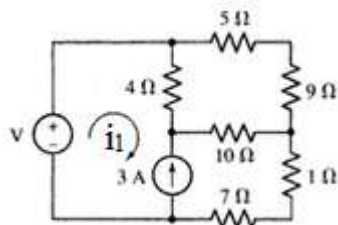


Figure-7

4. a) A $50 \mu\text{F}$ capacitor is connected in parallel with a choke coil which has a resistance of 20Ω and an inductance of 0.05 H across a 200V , 50 Hz supply. Calculate the total Current, branch current, power factor and active power of the circuit. 8 M
- b) A series RLC circuit has an impedance of 40Ω at a frequency of 200 rad/s . When the circuit is excited by a 10V source of variable frequency, the circuit resonates at 250 rad/s . The current at resonance is 0.5A and quality factor at resonance is 10 . Determine the circuit parameters. 8 M
5. a) Derive an expression for the total power input for a balanced 3-phase load in terms of line voltage, line current and power factor. 8 M
- b) Three inductive coils each of resistance 10Ω and reactance 6Ω are delta connected to a three phase, 415 V , 50Hz supply. Calculate i) line current, ii) power factor iii) power input to the circuit. 8 M
6. a) Explain the method of analyzing three phase unbalanced circuits by star-delta transformation technique. 8 M
- b) The following impedances are connected in the form of star connected unbalanced system and it is connected to a 400V , 3 phase supply; $Z_R=40\Omega$, $Z_Y=J24\Omega$, $Z_B= - J15\Omega$. Calculate the line currents by using i) loop method ii) star-delta transformation technique. 8 M