

Code: EC2T5

**I B.Tech - II Semester - Regular / Supplementary Examinations
May 2017**

**ELECTRONIC DEVICES & CIRCUITS
(ELECTRONICS & COMMUNICATION ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

PART – A

Answer *all* the questions. All questions carry equal marks

11x 2 = 22 M

1.

- a) Define
 - i) Magnetic field intensity
 - ii) Electric field intensity
- b) Draw the Energy band diagram of PN diode.
- c) Explain Avalanche Break down mechanism in diodes.
- d) Define
 - i) Efficiency
 - ii) Form factor of Rectifier.
- e) Draw the circuit diagram of Bridge Rectifier.
- f) Describe the Early effect of Transistor.
- g) Establish the relation between α and β of transistor.
- h) Draw Fixed bias circuit of CE Transistor.
- i) Give two applications of Photo Transistor.
- j) Define two Stability Factors.
- k) What is the advantage of self biasing circuit.

PART – B

Answer any **THREE** questions. All questions carry equal marks.

3 x 16 = 48 M

2. a) Derive the expression for transit time, and final velocity in the case of an electron traversing in uniform electric field. 8 M
- b) An electron with a velocity of $3 \times 10^5 \text{ ms}^{-1}$ enters an electric field of 910 v/m making an angle of 60° with the positive y direction. The direction of the electric field is in the positive Y direction. Calculate the time required to reach its maximum height. 8 M
3. a) Explain the operation of Zener diode with V-I Characteristics. 8 M
- b) Explain Principle of Operation and characteristics of Varactor Diode. 8 M
4. a) Derive the expression for ripple factor and efficiency of Full wave Rectifier. 8 M
- b) A Full wave rectifier circuit uses two Silicon diodes with a forward resistance of 20Ω each. A DC voltmeter connected across the load of $1 \text{ K}\Omega$ reads 55.4 volts. Calculate: 8 M

- i) I_{rms}
- ii) Peak Inverse Voltage across each diode.
- iii) Ripple factor.
- iv) Transformer Secondary Voltage rating.

5. a) Explain the operation of N-channel JFET and also draw Drain Characteristics. 8 M

b) Define R_d , g_m and μ of JFET and establish the relation between them. 8 M

6. a) Derive the expression for stability factor of collector to base bias circuit. 8 M

b) In collector to base bias method, An NPN Transistor if $\beta=50$ is used in common emitter circuit with $V_{CC}=10\text{ V}$, $R_C=2\text{K}\Omega$, and $R_B=100\text{K}\Omega$, Determine the Operating point. 8 M