

Code: CS2T4, IT2T2

**I B.Tech-II Semester-Regular Examinations - July 2013****DIGITAL LOGIC DESIGN****(For Computer Science & Engineering, Information Technology)**

Duration: 3 hours

Marks: 5x14=70

Answer any FIVE questions. All questions carry equal marks

1. a) Convert the following to Decimal and then to Hexadecimal

(i)  $(576)_8$

(ii)  $(4053)_8$

(iii)  $(11011011)_2$

(iv)  $(10111101)_2$

8 M

b) State and prove De-Morgan's Laws

6 M

2. a) Simplify the following Boolean functions algebraically

(i)  $(x+y)(x+y')$

(ii)  $(A+B')(A'+B')$

(iii)  $AB+A(CD+CD')$

(iv)  $A'B+ABC'+ABC$

8 M

b) Express the following functions in sum of minterms and product of maxterms

(i)  $F(A,B,C,D) = (AB + AC' + B'D + CD')$

(ii)  $F(x,y,z) = (x+yz)(xy+z)$

6 M

3. a) Simplify the following Boolean function and draw the logic circuit using NOR gates only

$$F(A,B,C,D) = \sum(0,1,2,3,7,8,10) + d(5,6,11,15)$$

7 M

- b) Simplify the following Boolean function and draw the logic circuit using NAND gates only  
 $F(A,B,C,D) = \prod(2,3,4,5,7,11,14,15)$  7 M
4. a) Design a Full adder and draw the logic diagram. 7 M
- b) Design a Full subtractor and realize the logic circuit. 7 M
5. a) What is a multiplexer? Draw 4X1 Multiplexer and explain. 7 M
- b) Design a BCD to Excess-3 code converter. 7 M
6. Draw and explain the block diagram of PLA.  
 Tabulate the PLA programmable table for the four Boolean functions
- $$A(x,y,z) = \sum m(0,2,3,5,7)$$
- $$B(x,y,z) = \sum m(0,1,4,6)$$
- $$C(x,y,z) = \sum m(1,4,6)$$
- $$D(x,y,z) = \sum m(0,2,3,7)$$
- 14 M
7. a) Draw the circuit diagram of clocked SR flip-flop and explain its operation. 7 M
- b) Draw the circuit diagram of clocked T flip-flop and explain its operation. 7 M
8. Design a mod -10 synchronous counter. 14 M