

Code: EE2T4

I B.Tech - II Semester – Regular Examinations – JULY 2015

**BASIC ELECTRONIC DEVICES AND CIRCUITS
(ELECTRICAL & ELECTRONICS ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

PART – A

Answer *all* the questions. All questions carry equal marks

11x 2 = 22 M

1. a) What is a PN junction? How is it formed?
- b) Define peak factor and ripple factor.
- c) Draw the symbols of photo diode, LED and Tunnel diode.
- d) What is meant by thermal stability? Give the condition for it.
- e) What is early effect?
- f) Advantages of negative feedback amplifier.
- g) Draw the V-I characteristics of Zener diode.
- h) Define stability factor.
- i) Define the condition for stability of an oscillator.
- j) Draw the transistor hybrid model.
- k) Differentiate JFET with BJT

PART – B

Answer any **THREE** questions. All questions carry equal marks. 3 x 16 = 48 M

2. a) Show that the zener diode can be used as a voltage regulator. 8 M

b) Draw the circuit diagram of a full wave rectifier. Explain the operation and derive the expression for I_{dc} , V_{dc} , I_{rms} and ripple factor. 8 M

3. a) Explain input and output characteristics of a Common Base configuration. 8 M

b) Explain the V-I characteristics of MOSFET in enhancement mode. 8 M

4. a) Derive an expression for the stability factor of a self bias circuit using transistor. 8 M

b) Explain in detail about the biasing of FET. 8 M

5. a) Compare the performance of a BJT as an amplifier in CE, CB & CC configurations. 8 M

b) Derive the parameters for high frequency BJT amplifiers and explain their interrelationship. 8 M

6. a) Draw the circuit of voltage series feedback amplifier and explain how stability is improved? Derive necessary equations.

8 M

b) State the barkhausen's criterion for stability and explain the Hartley oscillator operation with a neat sketch.

8 M