

Code: CS2T5, IT2T5

I B.Tech - II Semester – Regular Examinations – JULY 2015

BASIC ELECTRONICS ENGINEERING
(Common for CSE & IT)

Duration: 3 hours

Max. Marks: 70

PART – A

Answer *all* the questions. All questions carry equal marks

11x 2 = 22 M

1. a) Draw the volt-Ampere characteristics of PN Junction diode.
- b) List the applications of PN Junction diode.
- c) Draw the symbol of photo diode, Zener diode and LED
- d) What is meant by thermal runaway?
- e) Define ripple factor
- f) Define early effect in transistor CB configuration.
- g) Draw the block schematic of an OP-AMP
- h) Define Comparator.
- i) How is the slew rate measured?
- j) List the non ideal dc characteristics of an OP-AMP
- k) List out the applications of OP-AMP

PART – B

Answer any **THREE** questions. All questions carry equal marks. 3 x 16 = 48 M

2. a) Draw the energy band diagram of a PN junction and explain the working of a diode. 8 M
b) Explain the operation of zener diode as a voltage regulator 8 M
3. a) Show that a full-wave rectifier is twice as efficient as a half-wave rectifier. 8 M
b) List out the merits and demerits of Half-wave and full-wave rectifier. 8 M
4. Draw the circuit diagram of an NPN junction transistor CE configuration and describe the static input and output characteristics. Also defines active, saturation and cutoff regions. 16 M
5. List and explain the parameters given in manufacturer's data sheet of an OP-AMP 16 M
6. Explain with neat circuit of Inverting and Non Inverting amplifier using OP-AMP. 16 M