

Code: CE2T5, ME2T5

**I B.Tech - II Semester – Regular/Supplementary Examinations
April - 2019**

**BASIC ELECTRICAL & ELECTRONICS
ENGINEERING
(Common for CE & ME)**

Duration: 3 hours

Max. Marks: 70

PART – A

Answer *all* the questions. All questions carry equal marks

11x 2 = 22 M

1.

- a) Explain the conventional sources of energy.
- b) Develop the layout of solar power plant.
- c) Define Ohm's law.
- d) Analyze the Kirchoff's voltage law with an example.
- e) Draw slip torque characteristics of a 3- ϕ induction motor.
- f) Draw the circuit diagram of 1- ϕ capacitor start induction motor.
- g) Write an expression for regulation of 1- ϕ transformer.
- h) List the applications of DC welding generator.
- i) Explain the V- I characteristics of a P-N junction diode.
- j) Draw the circuit diagram of single stage CE amplifier.
- k) List out the different losses in a 1- ϕ transformer.

PART – B

Answer any **THREE** questions. All questions carry equal marks.
3 x 16 = 48 M

2. Explain the function of each component & operation of a gas turbine power plant with neat diagrams. 16 M

3. a) Obtain the expressions for equivalent resistance of a star-delta network transformations. 8 M

b) A resistance of 10 ohms is connected in series with two resistances of each 20 ohms arranged in parallel. If a voltage source of 40 V is connected across the circuit,

Determine: i) Total resistance.

ii) Total current.

iii) Current flow in each resistor.

iv) Power dissipated by each resistor.

8 M

4. a) A 6 pole, 3-phase, 50 Hz Induction motor has a full load speed of 950 rpm. Determine: 8 M

i) Synchronous speed ii) Slip speed

iii) Slip iv) Rotor frequency

- b) Explain the principle of operation of split phase induction motor. 8 M
5. a) Derive the EMF equation of a single phase transformer. 8 M
- b) List out the differences between AC and DC welding. 8 M
6. a) Explain the operation of half wave rectifier with neat diagrams. 8 M
- b) Explain the working of P-N-P transistor with neat diagrams. 8 M