

Code: CS2T5, IT2T5

**I B.Tech - II Semester – Regular/Supplementary Examinations
April - 2019**

**BASIC ELECTRONICS ENGINEERING
(Common for CSE & IT)**

Duration: 3 hours

Max. Marks: 70

PART – A

Answer *all* the questions. All questions carry equal marks

11 x 2 = 22 M

1.

- a) What is meant by intrinsic and extrinsic semiconductors?
- b) Describe the volt-ampere characteristics of a photodiode.
- c) A half wave rectifier is used to supply 24V DC to a resistive load of 500Ω and the diode has a forward resistance of 50Ω . Calculate the maximum value of the AC voltage at the input.
- d) Draw the circuit diagram of full wave rectifier with waveforms.
- e) Derive the relationship between α and β .
- f) Give the relation between I_C & I_{CEO} and between I_{CEO} & I_{CBO} .
- g) Draw the circuit diagram of closed loop non-inverting operational amplifier (OP-AMP).
- h) How does the slew rate measured?
- i) What is meant by PSRR?
- j) What are the applications of differentiator and integrator?
- k) Define Comparator.

PART – B

Answer any **THREE** questions. All questions carry equal marks.

3 x 16 = 48 M

2. a) Discuss the following with respect to semiconductor:
(i) doping (ii) dopant (iii) donor and (iv) acceptor 8 M
- b) Derive the conductivity equation for an N-type and P-type semiconductor. 8 M
3. a) Draw the circuit diagram of full-wave rectifier and explain its operation. 8 M
- b) A bridge rectifier with capacitor filter is fed from 220V to 40V step-down transformer. If average DC current to the load is 1A and capacitor filter of $800\mu\text{F}$, calculate the V_{rms} , I_{rms} , V_{dc} and ripple factor. Assume power line frequency of 50Hz, neglect diode forward resistance and DC resistance of secondary of transformer. 8 M
4. a) Explain how transistor is used as a switch. 8 M
- b) Explain the input and output characteristics of an NPN transistor in CB configuration. 8 M

5. a) Draw the basic internal block diagram of an op-amp and explain each block. 8 M
- b) State assumptions made for analyzing ideal op-amp and explain. 8 M
6. a) Explain the operation of op-amp as non-inverting amplifier. 7 M
- b) Explain the operation of op-amp as a differentiator. Plot the input and output waveforms by considering square wave as input. 9 M