

Code: EE3T5

II B.Tech - I Semester – Regular Examinations – December 2014

**ELECTRICAL CIRCUIT ANALYSIS - II**  
**(ELECTRICAL & ELECTRONICS ENGINEERING)**

Duration: 3 hours

Marks: 5x14=70

Answer any FIVE questions. All questions carry equal marks

- 1 a) Define various topological terms associated with graph of a network. 7 M
  
- b) Determine the value of  $I_1$  and  $I_2$  using general loop analysis for the circuit shown in Figure 1. 7 M

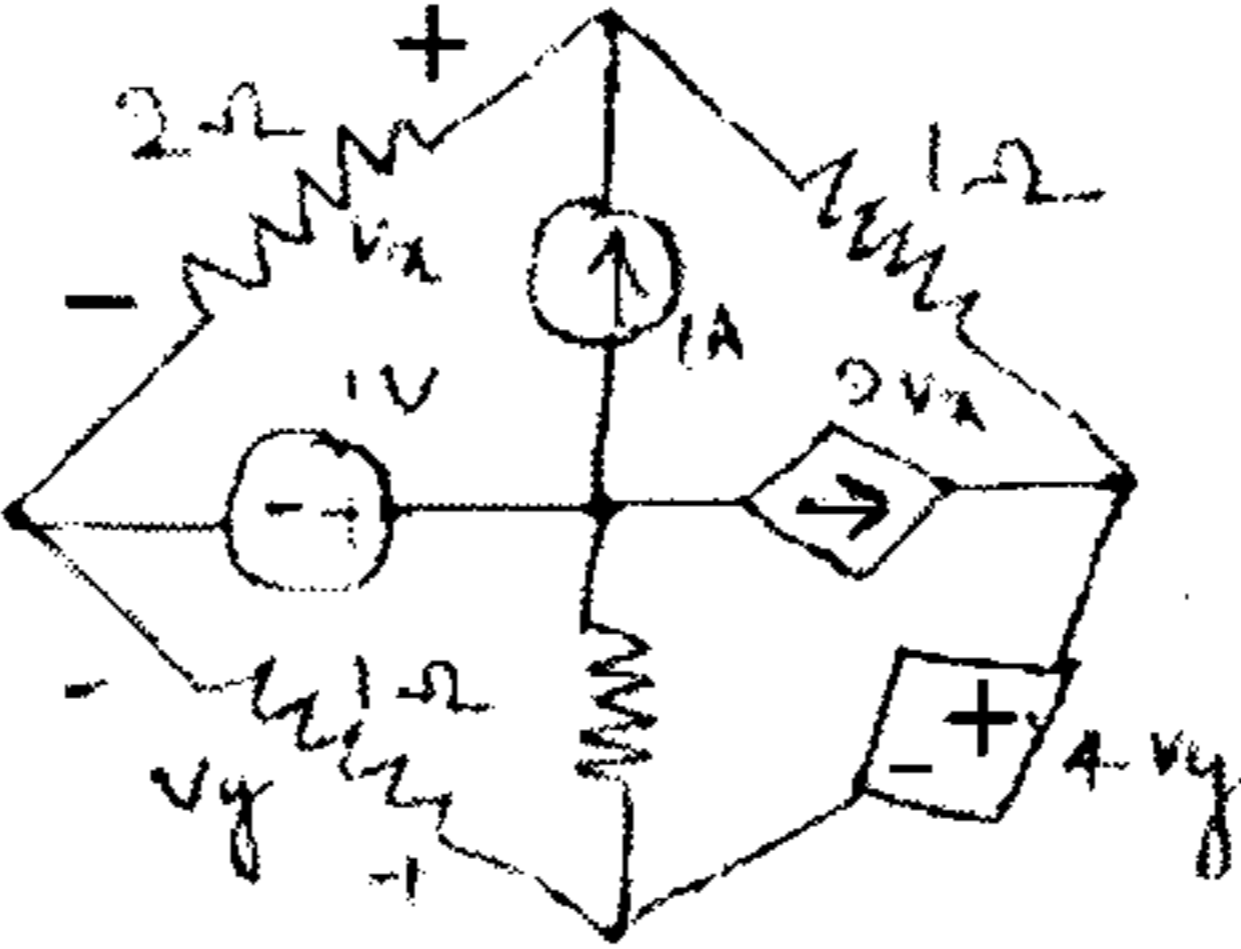


Figure 1

- 2 a) Define locus diagrams. Obtain the locus diagram of  $I$ ,  $V$ ,  $Z$  and power in a series R-L-C circuit. 7 M
  
- b) A simple RLC parallel circuit with  $R=500\Omega$ ,  $L=0.2H$  and  $C=375\mu F$  is excited by a current source of  $i(t) = 2 \cos 316t A$ . Determine  $R$ ,  $L$  and  $C$  values, resonant frequency, and band width and quality factor. 7 M

3 a) State and prove maximum power transfer theorem for circuits with ac excitation. 7 M

b) For the circuit shown in Figure 2, find the value of I using Thevenin's theorem. 7 M

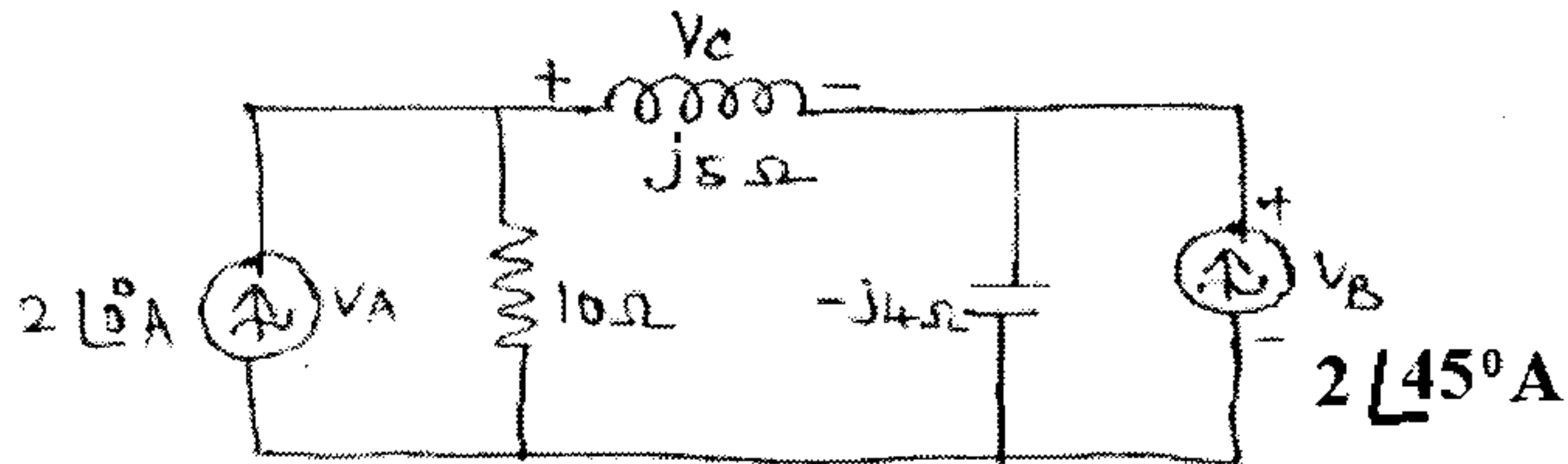


Figure 2

4 a) Explain the two-watt meter method of measuring power in a three phase balanced circuit feeding a balanced R-L load. 7 M

b) A balanced three phase, three wire system has Y-connected load containing a balanced three phase RLC load of  $50\Omega$ ,  $1.2\text{H}$  and  $50\mu\text{F}$  connected in series is fed by  $400\angle 0^\circ\text{ V}$  supply. Draw the phasor diagram of the line currents. 7 M

5 a) Explain the method of analyzing 3- $\emptyset$  unbalanced circuits by star – delta transformation technique. 7 M

b) Explain the two-watt meter method of determining 3- $\emptyset$  unbalanced loads fed by 3- $\emptyset$  balanced supply. How will you determine the power factor of the circuit by the readings of two watt meters? 7 M

6 a) Define and explain the properties of Laplace transforms. 7 M

b) Determine the inverse Laplace transform of  $\frac{e^{-s}(s+1)}{[(s+3)(s^2+2s)]}$  7 M

7 a) For the circuit shown in figure 3, the switch is closed at  $t=0$ . Find  $v_R$  when  $v_R = 10 \sin(100t + 45^\circ)V$ . 7 M

b) Explain the concepts of transient and natural responses. 7 M

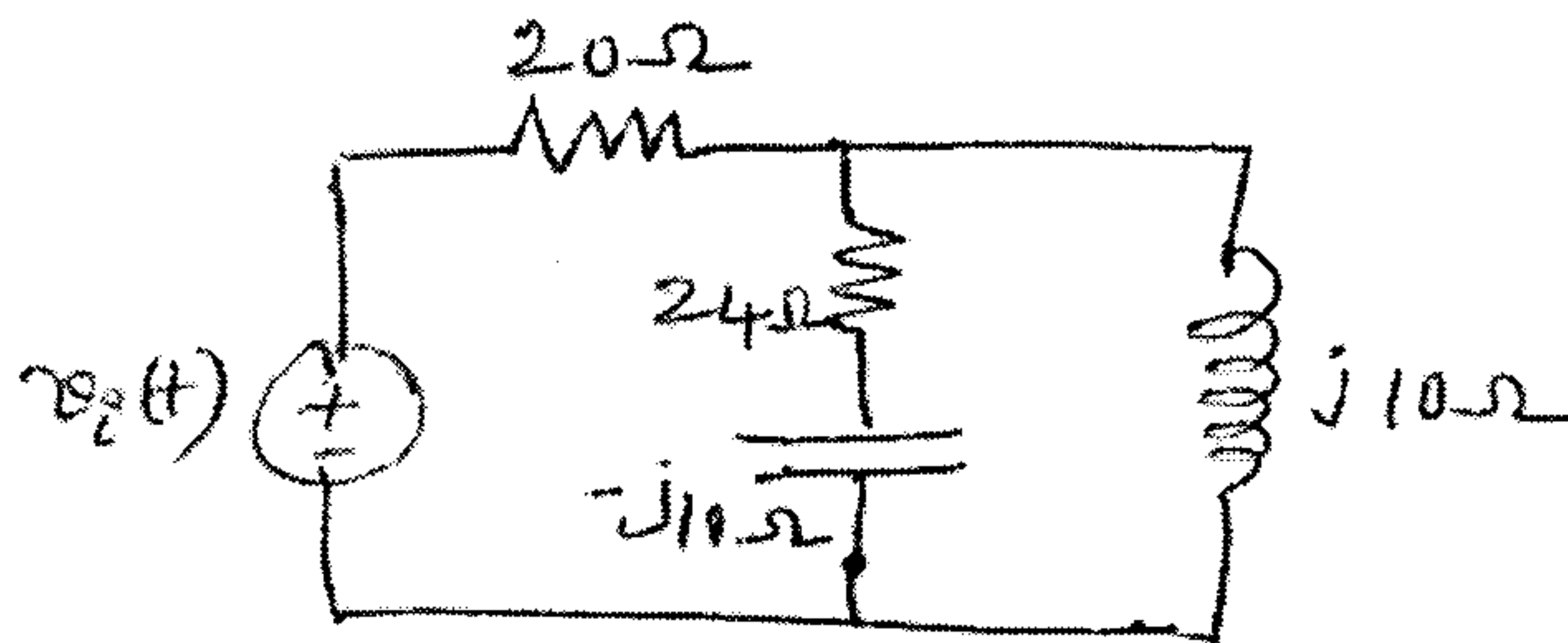


Figure 3

8 a) Obtain the trigonometric form of the Fourier series. 7 M

b) Using the Fourier transform method, find  $i_0$  in the circuit of Figure 4, at  $t=1$ , if  $v_s = \cos 2t$ . 7 M

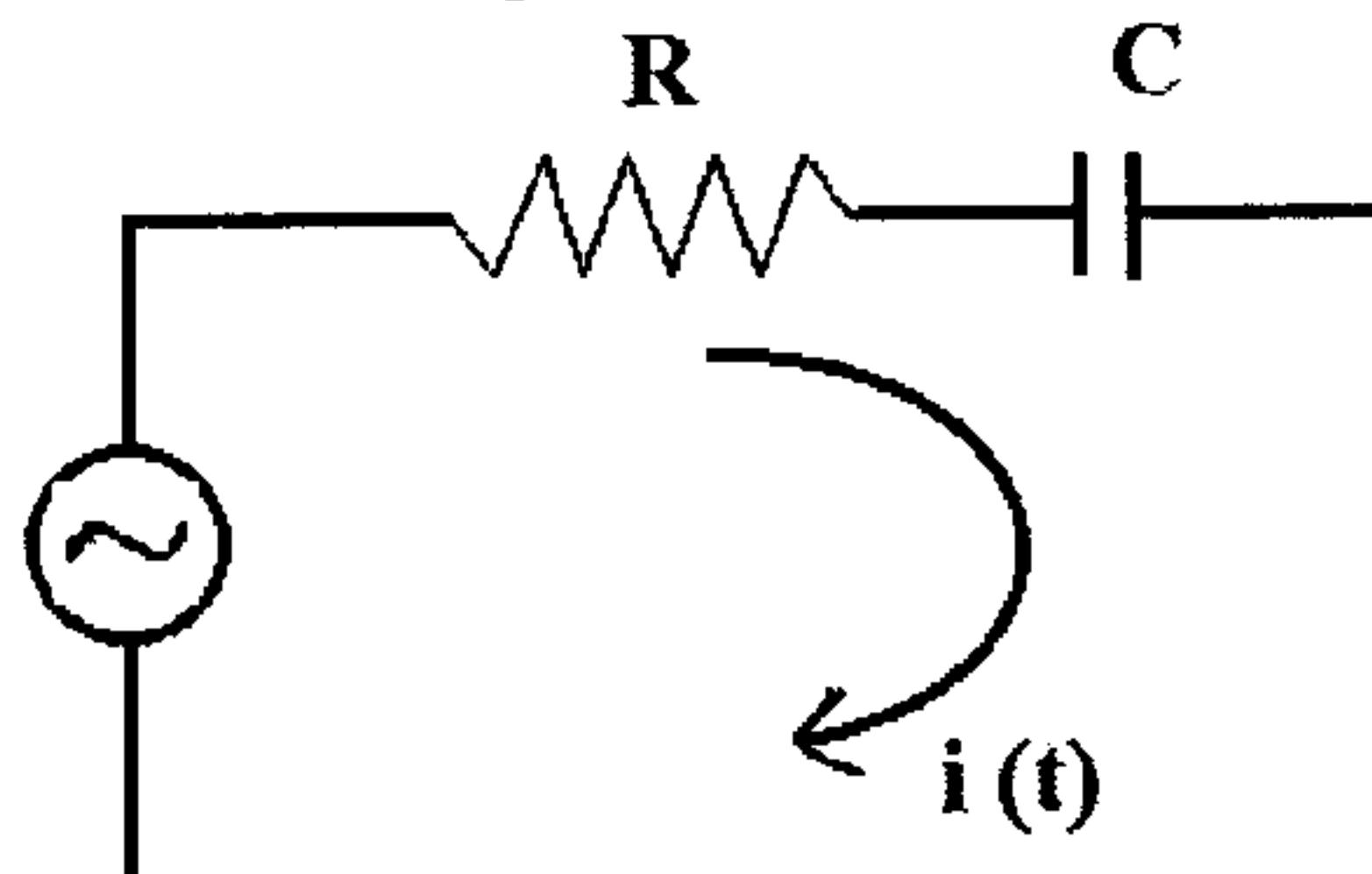


Figure 4