

Code: EE3T4

II B.Tech - I Semester – Regular Examinations – December 2015

**ELECTRICAL CIRCUIT ANALYSIS - II
(ELECTRICAL AND ELECTRONICS ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

PART – A

Answer *all* the questions. All questions carry equal marks


11x 2 = 22 M

1. a) State Ohm's Law.
- b) State Thevenin's Theorem.
- c) Write the relation between the Z and Y parameters of a Two-port network.
- d) What is the condition for symmetry in ABCD parameters?
- e) Write the condition for maximum power transfer theorem.
- f) State the final value Theorem.
- g) What do you understand by steady state stability?
- h) Write the Laplace transform of an Impulse signal and a Pulse Signal.
- i) What is the RMS and Average value of a sinusoidal waveform.
- j) What is Half-Wave symmetry?
- k) Draw the step response of an RC Circuit


PART – B

Answer any **THREE** questions. All questions carry equal marks. 3 x 16 = 48 M

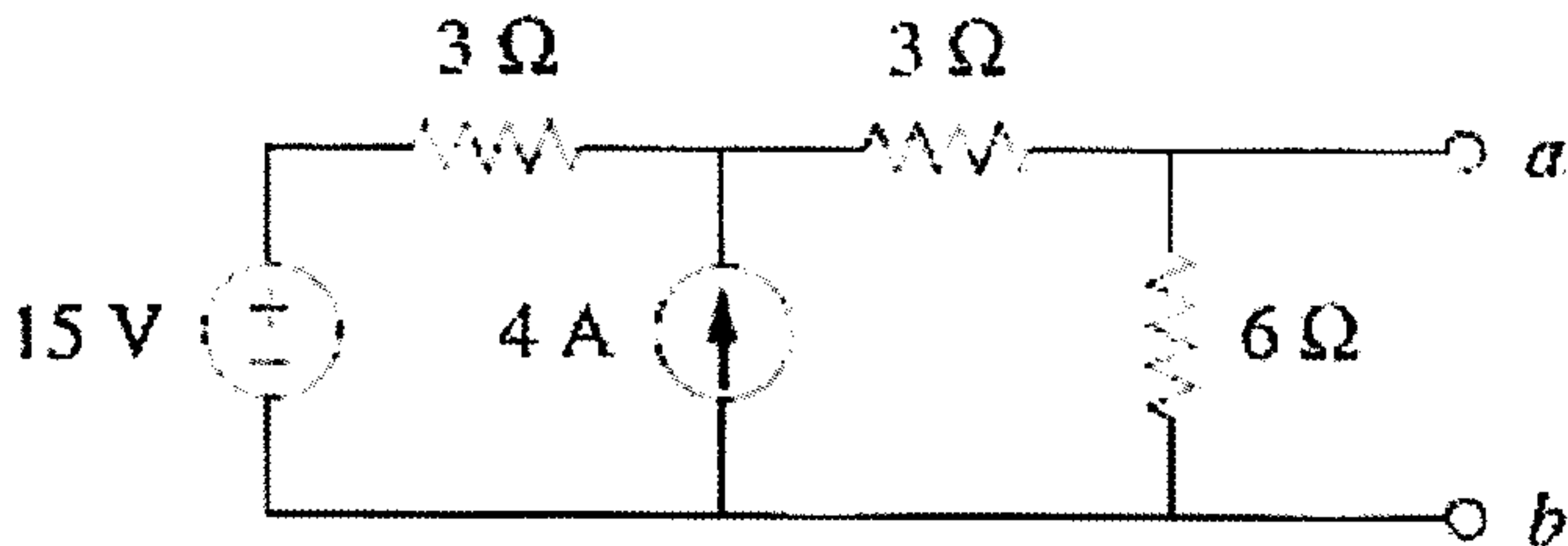2. a) Find the Norton equivalent circuit for the circuit shown in the figure at terminals a-b. 8 M




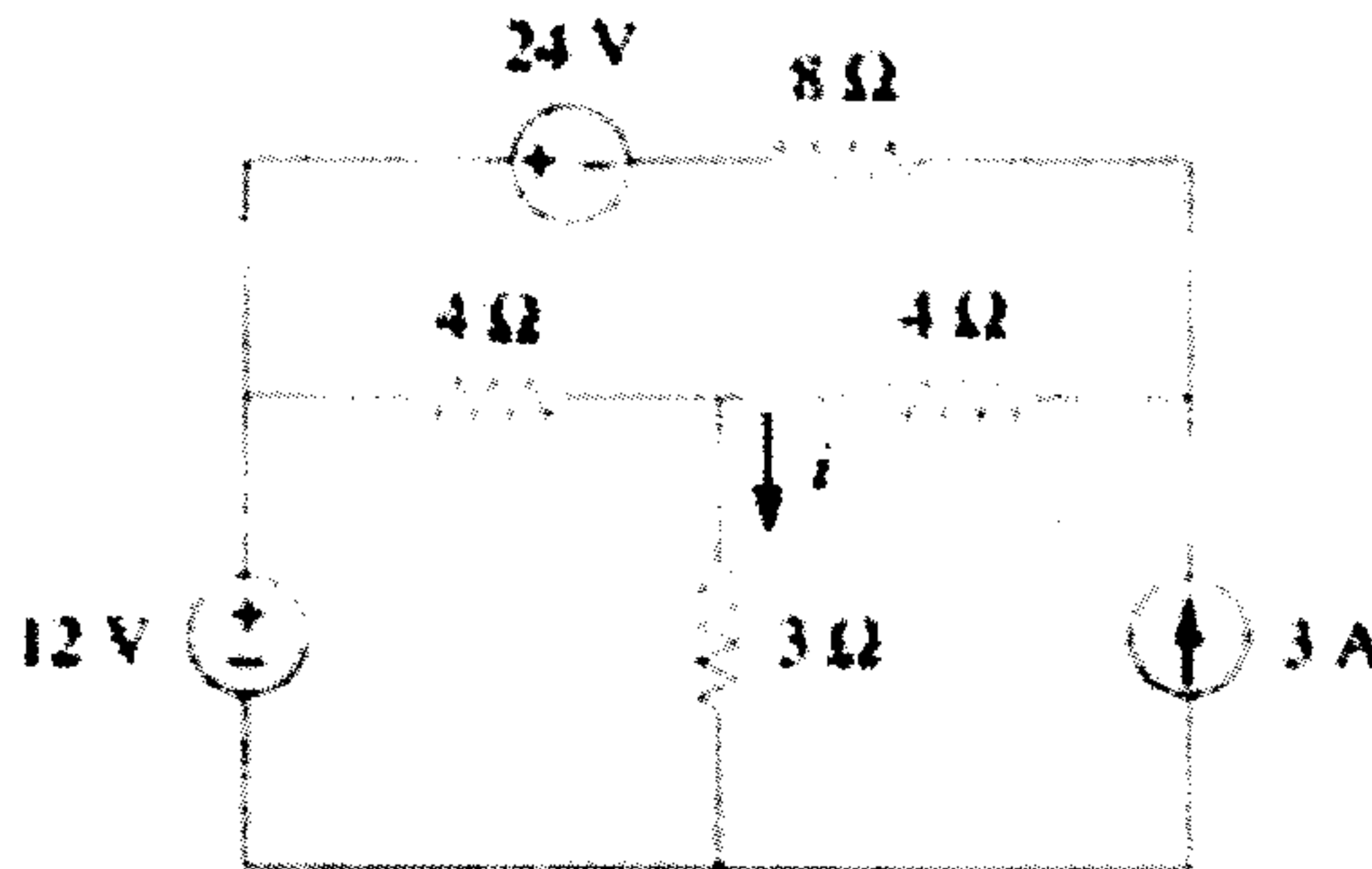- b) For the circuit shown below, use the superposition theorem to find the current i . 8 M



3. a) Determine the h parameters for the circuit shown below.


8 M

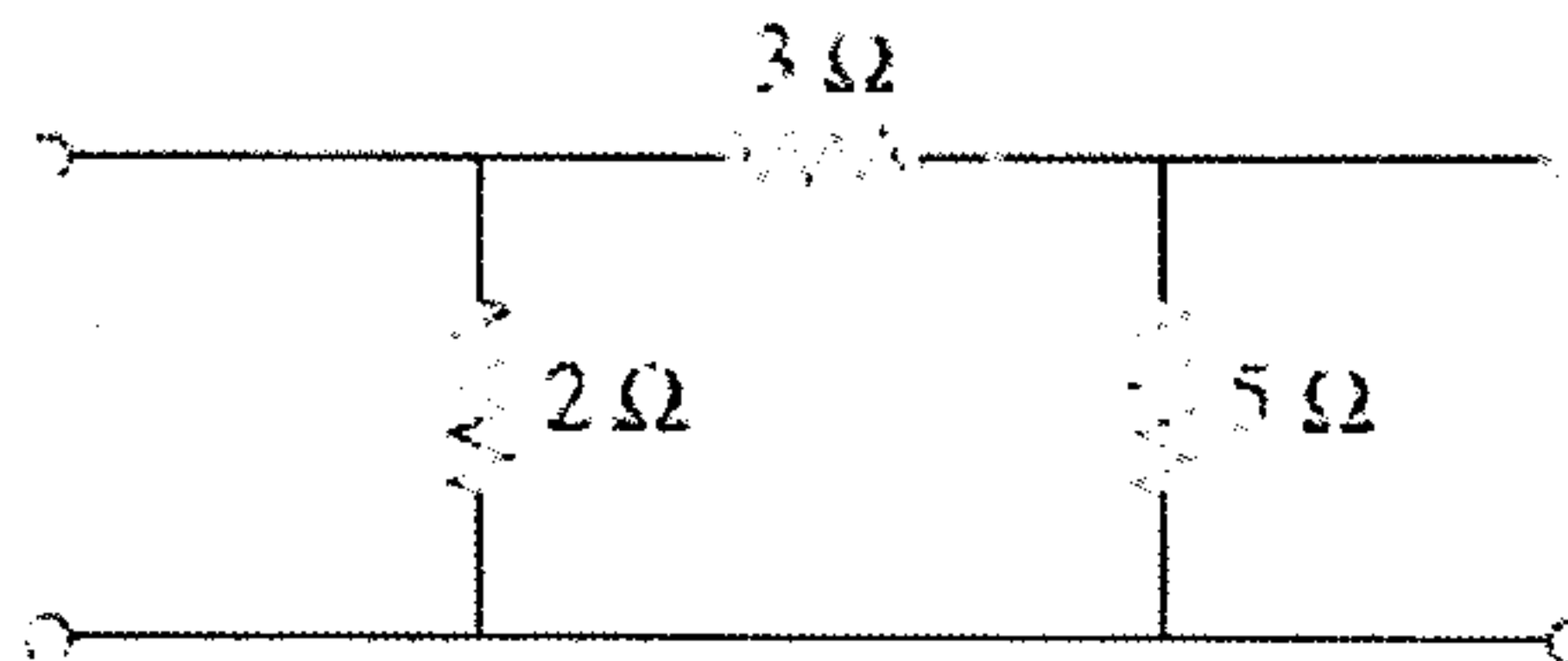

b) The Z parameters of a two-port network are $Z_{11}=10\Omega$, $Z_{22}=15\Omega$, $Z_{12}=5\Omega$, $Z_{21}=5\Omega$. Find the equivalent ABCD parameters. 8 M

4. a) Explain the properties of Laplace Transforms. 8 M

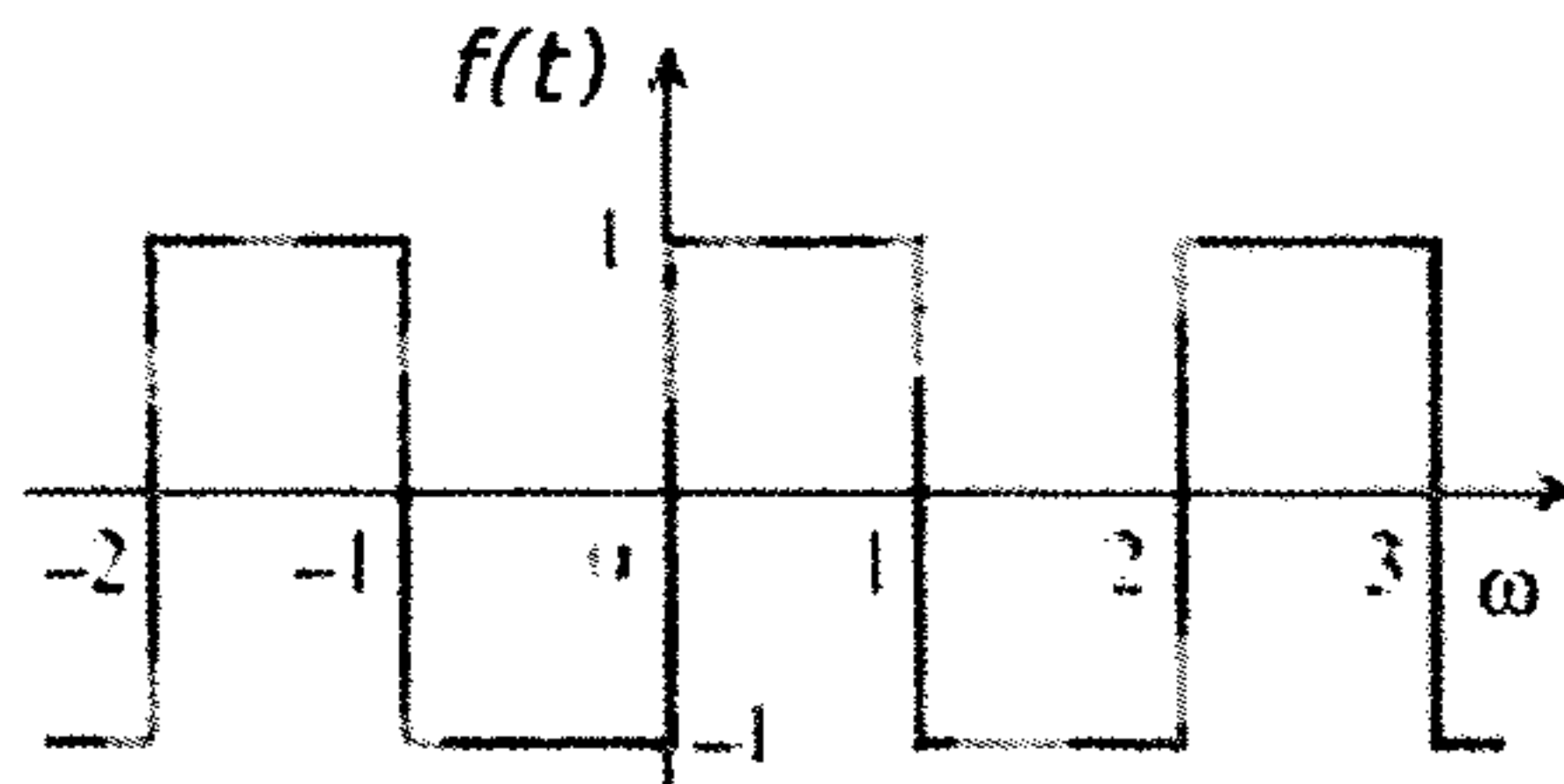
b) Find the Fourier series of the square wave. 8 M



5. a) Derive an expression for the step response of an R-C series circuit. Use Laplace transform approach. 8 M

b) Find the response of RL circuit for pulse input. 8 M

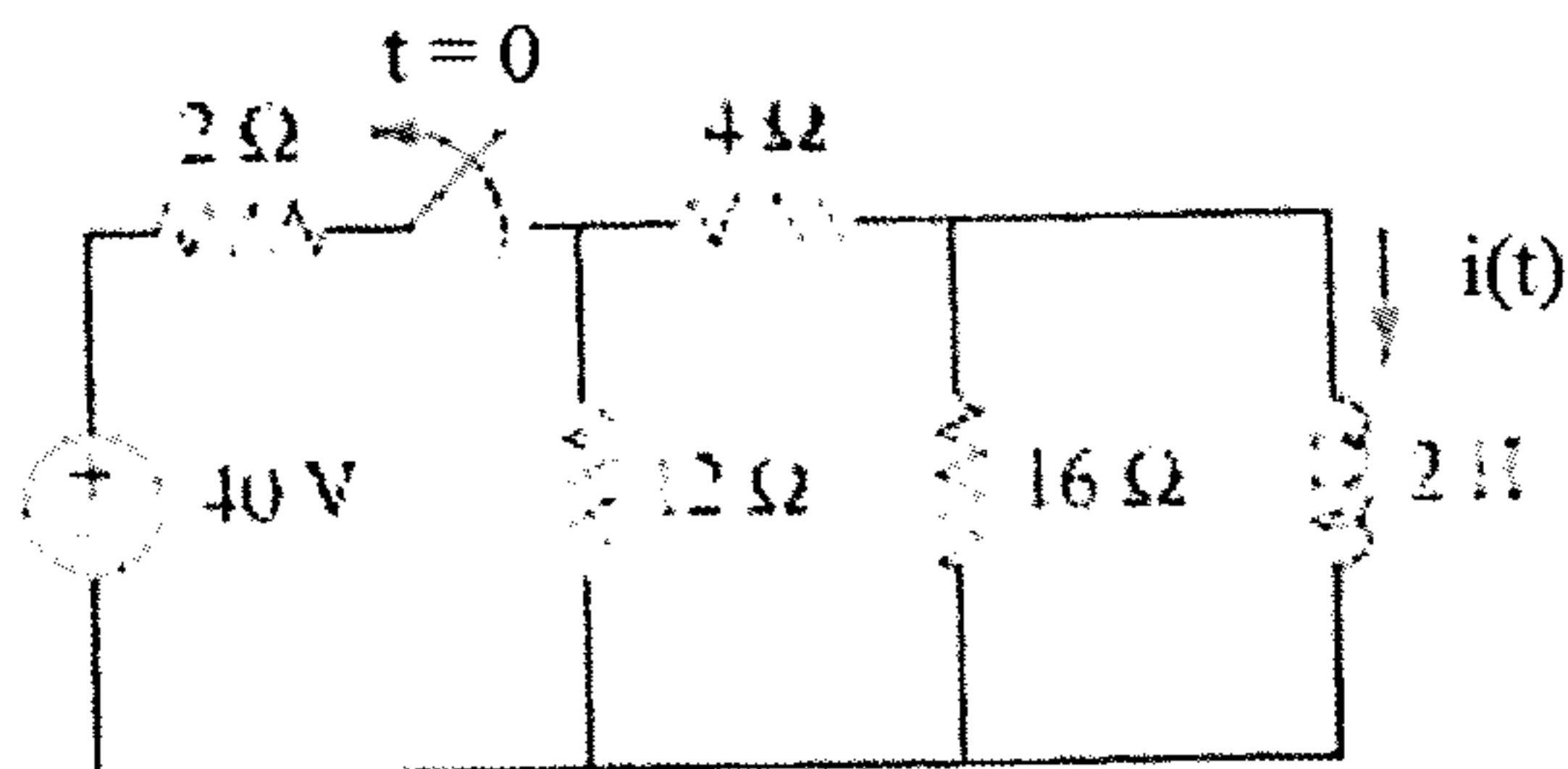6. a) The switch in the circuit has been closed for a long time. At $t = 0$, the switch is opened. Calculate $i(t)$ for $t > 0$. 8 M



b) For an RC series circuit, a sinusoidal voltage of $V(t) = V_m \sin(\omega t + \theta)$ is applied at $t=0$. Find the expression for $i(t)$ for $t > 0$.

8 M