

Code: 20EE3301, 20EC3301

**II B.Tech - I Semester – Regular/Supplementary Examinations
DECEMBER 2023**

**ELECTRONIC DEVICES AND AMPLIFIER CIRCUITS
(Common for EEE, ECE)**

Duration: 3 hours


Max. Marks: 70

Note: 1. This paper contains questions from 5 units of Syllabus. Each unit carries 14 marks and have an internal choice of Questions.
2. All parts of Question must be answered in one place.

BL – Blooms Level

CO – Course Outcome

			BL	CO	Max. Marks
UNIT-I					
1	a)	Describe the simplified structures and modes of operation of NPN transistor.	L2	CO1	7 M
	b)	Measurement of an NPN BJT in a particular circuit has the base current to be 14.46 μ A, the emitter current to be 1.460 mA and the base-emitter voltage to be 0.7 V. For these conditions, calculate α , β and I_S .	L3	CO2	7 M
OR					
2	a)	For the circuit shown below has $V_{cc}=V_I= + 5V$, $R_B = R_C = 1K\Omega$, and $\beta=100$. Calculate the base current, the collector current, and the collector voltage. If the transistor is saturated, find β_{forced} . What value should R_B be raised to in order to bring the transistor to the edge of saturation?	L3	CO2	7 M

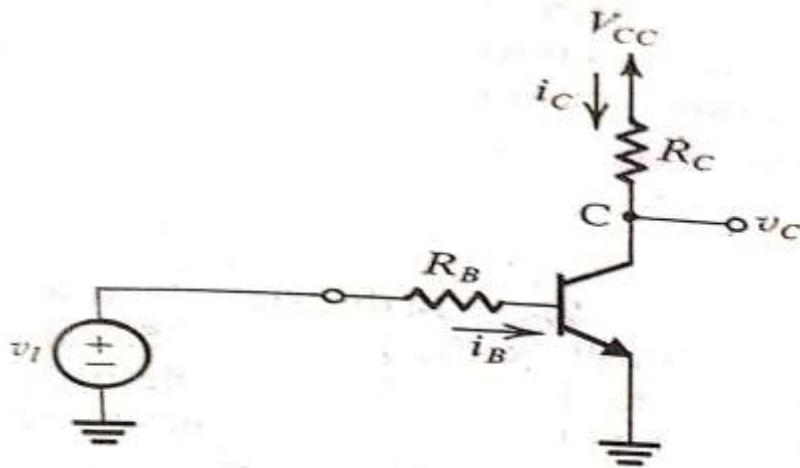

- b) Design the circuit for implementing the current source 'I' and analyze the operation of BJT biased using a constant-current source.

L4

CO4

7 M

UNIT-II

- | | | | | | |
|---|----|--|----|-----|-----|
| 3 | a) | Explain the i_d - V_{ds} relationship for the NMOS transistor and also sketch the characteristics. | L4 | CO1 | 7 M |
| | b) | Analyze the large signal operation and transfer characteristics of the CS Amplifier. | L4 | CO2 | 7 M |

OR

- | | | | | | |
|---|----|--|----|-----|-----|
| 4 | a) | It is required to design the below circuit to establish a dc drain current $I_D=0.5\text{mA}$. The MOSFET is specified to have $V_t=1\text{V}$ and $k'_n W/L = 1\text{mA/V}^2$. For simplicity, neglect channel length modulation $\lambda=0$. Consider $V_{DD}=15\text{V}$. Calculate the percentage change in the value of I_D obtained when the MOSFET is replaced with another unit having the same $k'_n W/L$ but $V_t=1.5\text{V}$. | L3 | CO2 | 7 M |
|---|----|--|----|-----|-----|

	b)	Draw and explain the small-signal operation of MOSFET amplifier.	L3	CO2	7 M

UNIT-III

5	a)	Derive voltage gain, open circuit voltage gain and overall voltage gain for common gate amplifier using small signal analysis.	L3	CO3	7 M
	b)	Analyze the short-circuit current gain and unity-gain frequency for CS amplifier using hybrid- π model.	L4	CO3	7 M

OR

6	a)	A CS amplifier has $C_{C1} = C_S = C_{C2} = 1\mu\text{F}$, $R_G = 10\text{M}\Omega$, $R_{\text{sig}} = 100\text{K}\Omega$, $g_m = 2\text{mA/V}$, $R_D = R_L = 10\text{K}\Omega$. Calculate $A_M, f_{P1}, f_{P2}, f_{P3}, f_L$.	L3	CO3	7 M
	b)	With the help of neat diagram explain capacitively coupled common source amplifier and sketch the frequency response including three frequency bands.	L2	CO3	7 M

UNIT-IV

7	a)	Obtain the Common-Mode gain and Common-mode Rejection ratio of MOS differential pair with small-signal operation.	L4	CO1	7 M
---	----	---	----	-----	-----

	b)	Explain the MOS differential pair operation with a differential input voltage.	L2	CO3	7 M
OR					
8	a)	Estimate the three components of the input offset voltage for the MOS differential pair having $V_{OV} = 0.2V$, $\Delta R_D/R_D=2\%$, $\Delta(W/L)/(W/L) = 2\%$ and $\Delta V_t = 2 \text{ mV}$.	L4	CO3	7 M
	b)	Illustrate the simple basic approach for differential-to-single ended conversion.	L3	CO1	7 M
UNIT-V					
9	a)	Consider a basic MOSFET constant current source circuit with $V_{DD} = 3V$, $I_{REF} = 100\mu A$ to obtain an output current whose value is $100\mu A$. Find R if Q_1 & Q_2 are matched & have channel length of $1\mu m$, channel width of $10\mu m$, $V_t = 0.7V$ & $k'_n=200\mu A/v^2$. What is the lowest possible value of V_O . Assume $V'_A = 20 \text{ v}/\mu m$. Calculate output resistance of the current source.	L3	CO4	7 M
	b)	Analyze the MOSFET current mirror circuit and derive current transfer ratio also sketch transfer characteristics.	L4	CO4	7 M
OR					
10	a)	Differentiate the MOSFET scaling techniques.	L4	CO1	7 M
	b)	Demonstrate the operation of MOS Current-Steering Circuit with neat sketch.	L2	CO4	7 M