

Code: 20ES1302

**II B.Tech - I Semester –Regular / Supplementary Examinations
DECEMBER 2023**

**CIRCUIT THEORY
(ELECTRICAL & ELECTRONICS ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

Note: 1. This paper contains questions from 5 units of Syllabus. Each unit carries 14 marks and have an internal choice of Questions.
2. All parts of Question must be answered in one place.

BL – Blooms Level

CO – Course Outcome


			BL	CO	Max. Marks
UNIT-I					
1	a)	An inductive coil takes 10A and dissipates 1000watts when connected to a supply of 250V, 25Hz. Calculate the (i) impedance (ii) effective resistance (iii) reactance (iv) inductance (v) power factor.	L3	CO2	7 M
	b)	For a load, $V_{rms} = 110\angle 85^{\circ}V$, $I_{rms} = 0.4\angle 15^{\circ}A$. Determine i) Active power ii) Reactive power iii) Apparent power.	L3	CO2	7 M
OR					
2	a)	A two element series circuit is connected across an AC source given by $v=200\sqrt{2}\sin(314t+20^{\circ})$. The current in the circuit is found to be $i=10\sqrt{2}\cos(314t-25^{\circ})$. Determine the parameters of the circuit. Also determine the power factor, real power and reactive power taken by the circuit	L3	CO2	7 M
	b)	What is impedance diagram? Derive the expression for impedance of a RLC series circuit.	L3	CO2	7 M

UNIT-II

3	a)	In a series resonant circuit prove that resonant frequency is the geometric mean of two half power frequencies.	L3	CO3	7 M
	b)	A series RLC circuit with $R= 100\Omega$, $L=0.5H$ and $C=40\mu F$ has an applied voltage of 50V with variable frequency. Calculate (i) Resonant frequency, (ii) Current at resonance, and (iii) Voltage across R, L and C	L3	CO3	7 M


OR

4	a)	Derive the relation between the resonance frequency and bandwidth of resonance circuit	L3	CO3	7 M
	b)	Verify reciprocity theorem for the network shown in the figure.	L3	CO3	7 M

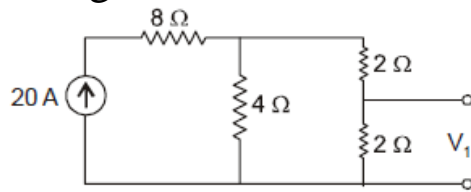


UNIT-III

5	a)	If $Z_{11} = 3 \Omega$, $Z_{12} = 2 \Omega$, $Z_{21} = 3 \Omega$ and $Z_{22} = 1 \Omega$, find the Y-parameters and ABCD parameters.	L3	CO2	7 M
	b)	Obtain the Y-parameters of a Two Port network shown in figure.	L4	CO5	7 M

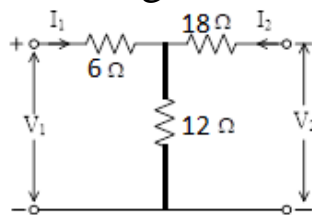

OR


6	a)	Determine h-parameters and impedance parameters for the following network.	L4	CO5	7 M
---	----	--	----	-----	-----

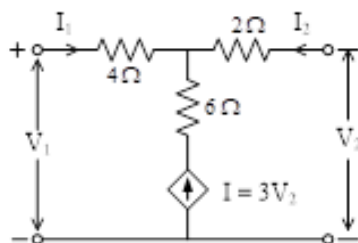


	b)	Derive the expression for Coefficient of Coupling.	L2	CO1	7 M
--	----	--	----	-----	-----

UNIT-IV

7	a)	In the following network switch K is closed at $t=0$ with zero current in the inductor. Find the values of i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t=0^+$.	L4	CO4	7 M
---	----	---	----	-----	-----

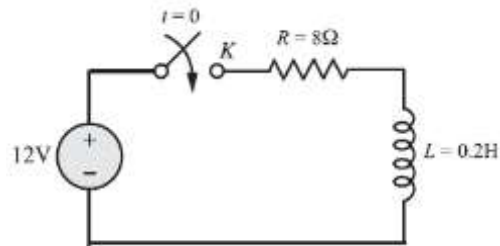



	b)	In the circuit shown in the figure, find the transient voltage across R and L after the switch is closed at time $t=0$. Assume the initial current through the inductor before the switch is closed.	L4	CO4	7 M
--	----	---	----	-----	-----

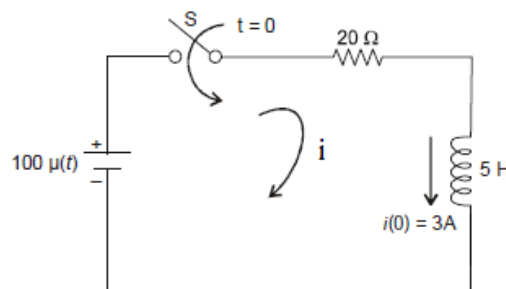

OR

8	a)	Derive the expression for $i(t)$ in the given circuit for $t>0$. assume that there is no charge on the capacitor and no current passing through the inductor initially	L4	CO4	7 M
---	----	---	----	-----	-----

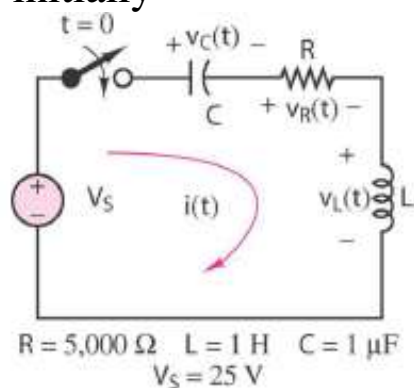

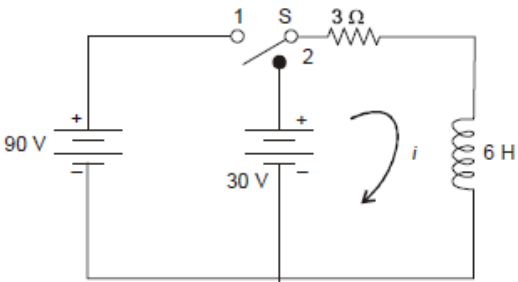	<p>b) In the circuit shown in the figure, switch 'S' is in position 1 for a long time and brought to position 2 at time $t=0$. Find the transient current.</p> 	L4	CO4	7 M
--	---	----	-----	-----

UNIT-V

9	<p>a) A 3-phase, 440V load has a power factor of 0.4. Two wattmeters are connected to measure the power. If the input power be 10 kW, find the reading of each instrument.</p>	L4	CO4	7 M
	<p>b) Develop Relation between line and phase voltages and currents in a delta connected 3-phase balanced system.</p>	L4	CO3	7 M

OR

10	<p>a) A balanced delta connected load of $(8 + j6) \Omega$ per phase is connected to a 3-phase, 50 Hz, 230V supply. Calculate (i) Line current (ii) Reactive volt-ampere, (iii) power factor, and (iv) Total volt-ampere.</p>	L4	CO4	7 M
	<p>b) Two wattmeters are used to measure power input to a 1.5kV, 50 Hz, 3-phase motor running on full load at an efficiency of 85%. Their readings are 250kW and 80kW respectively. Calculate (i) input power (ii) Power factor, and (iii) Line current</p>	L4	CO4	7 M