

UNIT – II

3. a) Reduce the following expressing using K-map
- i) $(A+B) (A+\bar{B}+C) (A+\bar{C})$
 - ii) $A(B+\bar{C}) (A+\bar{B}) (B+C+\bar{D})$
- 7 M
- b) Reduce the following expression
- $$F = \sum m (2,3,6,7,8,10,11,13,14)$$
- and implement it using NOR Gates.
- 7 M
- OR
4. a) Realize the XOR function using
- i) AOI logic
 - ii) NAND logic
- 7 M
- b) Reduce the following expression
- $$F = \prod M (2,8,9,10,11,12,14)$$
- and implement it in universal logic.
- 7 M

UNIT-III

5. a) Design a 4-bit binary to BCD converter.
- 7 M
- b) Implement the logic function using an 8 X 1 Multiplexer.
- $$F (A, B, C, D) = \sum m (1,3,4,11,12,13,14,15)$$
- 7 M
- OR
6. a) Give the necessary logical circuit for carry generation in Carry-Look-Ahead adder.
- 7 M
- b) Design a Full Adder circuit and realize it using two half adders.
- 7 M

UNIT – IV

7. a) Convert the S-R flip-flop to J-K flip-flop using conversion table and implement the logic diagram. 7 M
b) Explain the SR flip flop with necessary diagrams. 7 M

OR

8. a) Distinguish between JK flip-flop and Master Slave JK flip-flop. 7 M
b) Convert the J-K flip-flop to S-R flip-flop using conversion table and implement the logic diagram. 7 M

UNIT – V

9. a) Design a Mod-9 Synchronous counter using T- FF. 7 M
b) With neat diagram explain the 4-bit Serial-in, Parallel-out shift Register. 7 M

OR

10. a) Design an up/down counter using D FF's to count 0,3,2,6,4,0 7 M
b) What is universal shift register and explain with neat diagram. 7 M