

Code: 19EE3301

II B.Tech - I Semester – Regular Examinations – MARCH 2021**ELECTRICAL CIRCUIT ANALYSIS
(ELECTRICAL AND ELECTRONICS ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

-
- Note: 1. This question paper contains two Parts A and B.
2. Part-A contains 5 short answer questions. Each Question carries 2 Marks.
3. Part-B contains 5 essay questions with an internal choice from each unit. Each question carries 12 marks.
4. All parts of Question paper must be answered in one place
-

PART – A

1. a) Define Reactive Power.
- b) State Millman's Theorem.
- c) What is the Final condition of the elements Inductor & Capacitor, when the switch is closed for long time?
- d) Define Co-efficient of coupling.
- e) Compare Single Phase System and Three Phase System.

PART – B**UNIT – I**


2. a) Briefly Explain about (i) Power Factor (ii) Power Triangle (iii) Complex Power. 6 M
- b) A sinusoidal voltage $v(t)=50\sin(314t)$ volts is applied to an AC circuit. The current is $i(t)=25\sin(314t-53^\circ)$ amperes. Determine (i) Average Power (ii) Apparent Power (iii) Power Factor. 6 M

OR

3. a) Explain the steady state analysis of Series RC circuit 6 M
when excited by a sinusoidal input.
- b) Determine the steady state current in a Series RL circuit 6 M
which consists of $R=20\Omega$, $L=0.1H$ when excited by a
voltage $v(t)=100\cos(1000t+90^\circ)$ volts.


UNIT – II

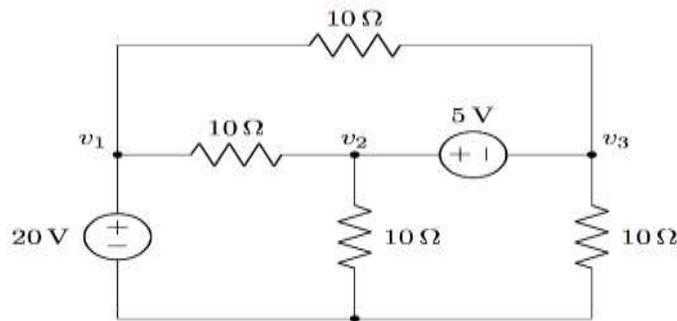4. a) Briefly discuss about (i)Series Resonance (ii)Parallel
Resonance. 6 M
- b) Determine the node voltages of given circuit using 6 M
Super Node Analysis.




OR

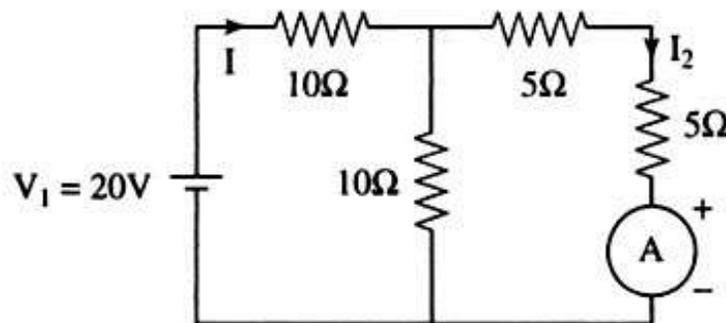5. a) State and prove Tellegen's Theorem with an example. 6 M
- b) Verify Reciprocity Theorem for the given circuit. 6 M



UNIT-III

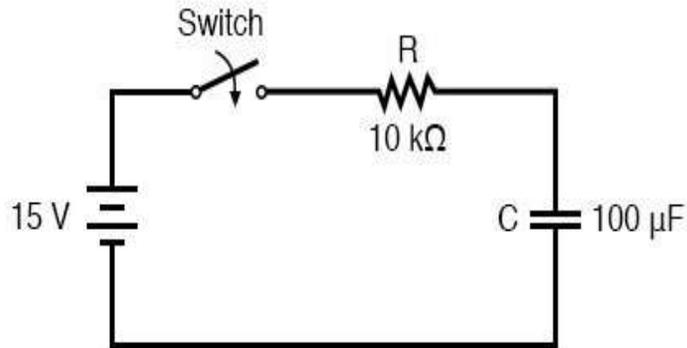6. a) Derive an expression for Step Response of Series RLC Circuit. 6 M
- b) For the given Series RC Circuit, determine the current in the circuit when the voltage is applied by closing the switch at $t=0$. 6 M




OR

7. For a Series RL circuit, a sinusoidal voltage is applied at $t=0$. Determine the expression for $i(t)$ for $t > 0$. 12 M


UNIT – IV

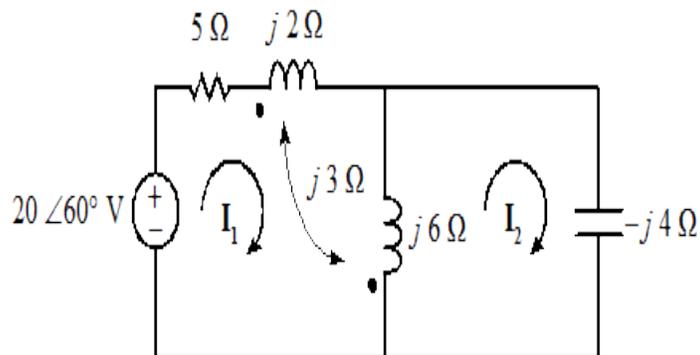8. a) Explain in brief about (i) Self Inductance (ii) Mutual Inductance. 6 M
- b) Determine the Loop Currents I_1 and I_2 in the given circuit. 6 M



OR

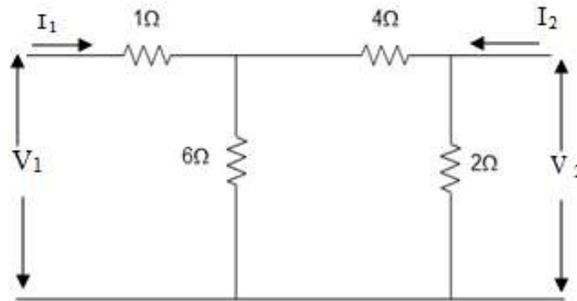9. a) The impedance parameters of a two port network are 6 M
 $Z_{11}=6\Omega$, $Z_{22}=4\Omega$, $Z_{12}=Z_{21}=3\Omega$. Compute the
Admittance Parameters and Transmission Parameters.
- b) Find the Hybrid Parameters for the given two port 6 M
network.



UNIT – V

10. a) Explain about Star Connected three phase balanced 6 M
system and derive the relationship between line and
phase voltages.
- b) A balanced Delta Connected load of $(2+j3)\Omega$ per phase 6 M
is connected to a balanced three phase supply of 440V.
Determine the phase currents and line currents.

OR

11. a) Explain the two wattmeter method to measure the 6 M
power in three phase circuits.
- b) The input power to a three phase load is 10kW at 0.8 6 M
power factor lagging. Two wattmeters are connected to
measure the power. Find the individual readings of the
wattmeters.