

Code: EE3T4

**II B.Tech - I Semester–Regular/Supplementary Examinations
November 2016**

**ELECTRICAL CIRCUIT ANALYSIS - II
(ELECTRICAL AND ELECTRONICS ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

PART – A

Answer *all* the questions. All questions carry equal marks

11x 2 = 22 M

1.

- a) State Compensation's theorem.
- b) State Tellegen's theorem.
- c) Write the relation between Z and Hybrid (H) parameters.
- d) Prove the reciprocity condition of ABCD parameters.
- e) State and express the initial value theorem.
- f) Write dirchilet conditions.
- g) Express the Fourier series coefficients of even function symmetry.
- h) Find voltage across capacitance in a series R-C circuit having $R=5\Omega$ and $C=0.1F$ with 5V DC excitation applied at $t=0$.
- i) Find $i(t)$ in a series R-L circuit having $R=25\Omega$ and $L=2H$ with 50V DC excitation applied at $t=0$.
- j) Express the current $i(t)$ of a R-L-C series circuit is energised with dc source in under damped condition.

k) Find the condition for critical damping in a R-L-C series circuit.

PART – B

Answer any **THREE** questions. All questions carry equal marks.
 $3 \times 16 = 48 \text{ M}$

2.

a) Find current I_y in 5Ω resistor using superposition theorem for the circuit shown in Fig. 1. 8 M

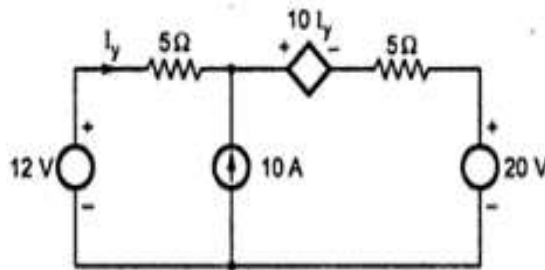


Fig. 1

b) Find the current through PQ branch for the circuit shown in Fig. 2. 8 M

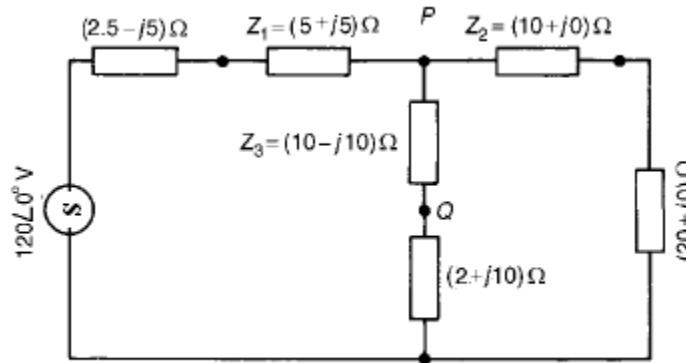


Fig. 2

3.

a) Obtain ABCD parameters for the network shown in Fig. 3. 8 M

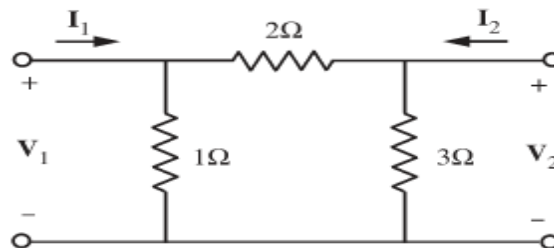


Fig. 3

b) Obtain Z-parameters for the network shown in Fig. 4.

8 M

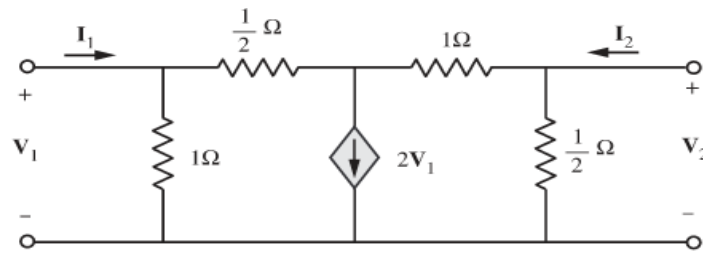


Fig. 4

4.

a) Find the Fourier series expansion of the wave form shown in Fig. 5.

8 M

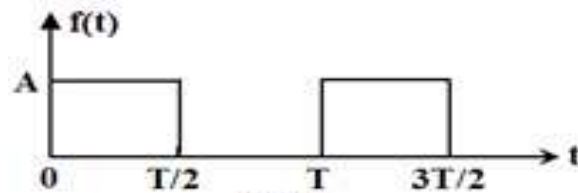


Fig. 5

b) Obtain the exponential Fourier series expansion for the signal shown in Fig. 6.

8 M

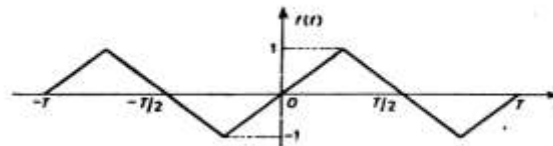


Fig. 6

5.

a) Derive the equation for the transient current $i(t)$ in a series RL circuit excited by a step input of V volts, at time $t=0$. Assume zero initial current for the inductor.

8 M

- b) The switch shown in the Fig. 7 is moved from position A to B at $t=0$. Determine $i(t)$ and $i(t)$ at $t=2$ mS. 8 M

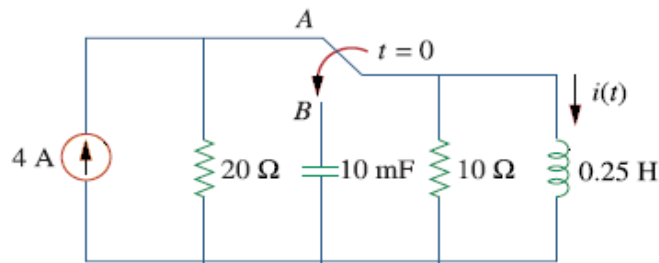


Fig. 7

6.

- a) Derive the equation for the transient current $i(t)$ in a series RC circuit excited by a sinusoidal voltage source $v(t) = V_m \sin \omega t$, at time $t=0$. Assume zero initial charge across the capacitor. 8 M
- b) A series RLC circuit with $R=2 \Omega$, $L=1$ H and $C= 1$ F has a sinusoidal voltage source $v(t) = 250 \text{ Sin } 500t$ applied at time $t=0$. Determine the transient current $i(t)$. Assume zero initial conditions. 8 M