

Code: EE3T4

**II B.Tech - I Semester–Regular/Supplementary Examinations –
November 2017**

**ELECTRICAL CIRCUIT ANALYSIS - II
(ELECTRICAL AND ELECTRONICS ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

PART – A

Answer *all* the questions. All questions carry equal marks


11x 2 = 22 M

1. a) What is the condition for transfer of maximum power from source to load?
- b) State Tellegen's theorem.
- c) Write the relations for open circuit parameters.
- d) What is the driving point impedance?
- e) What are the hybrid parameters?
- f) State final value theorem.
- g) State the representation of Trigonometric form of Fourier series.
- h) Define the even function symmetry with examples.
- i) Define the time constant.
- j) A dc voltage is applied in RC circuit where $R=10\Omega$ and $C=0.02\mu\text{F}$. Find the time constant.
- k) What are the causes of occurring the transients in electrical circuits.


PART – B

Answer any **THREE** questions. All questions carry equal marks.
 $3 \times 16 = 48 \text{ M}$

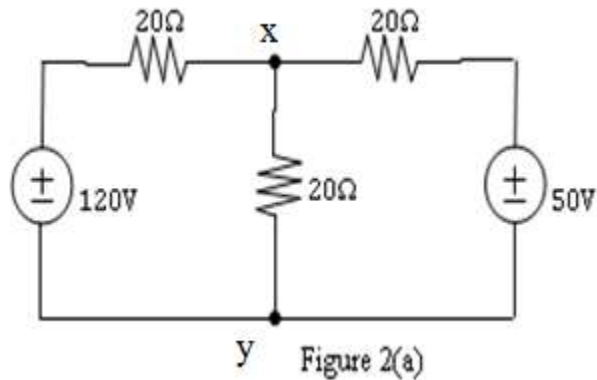
2. a) Using Superposition theorem, find the current through x-y branch in the circuit of figure 2(a). 8 M



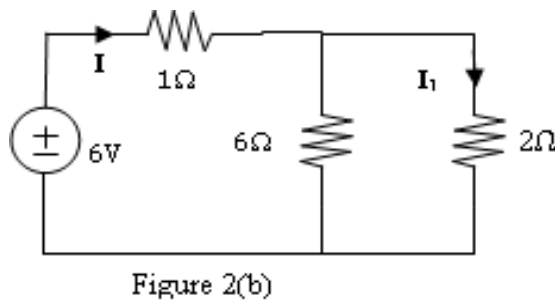- b) Find the current flowing through 2Ω resistor in the circuit shown in figure 2(b) and verify the Reciprocity theorem. 8 M



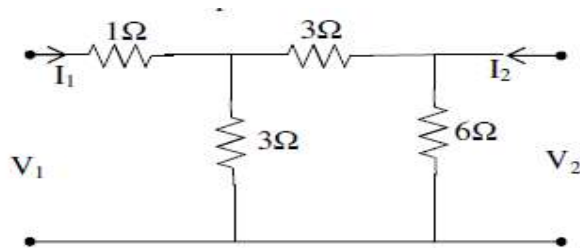3. Determine the Z-parameters and Y-parameters for the network shown below Figure 3. 16 M



4. a) Find the expression $i(t)$ of series RLC circuit with $R= 5\Omega$, $L= 1H$, $C= 1/4F$, when it is fed by a ramp voltage of $12r(t-2)$. 8 M

b) A voltage $v(t) = 1000 \sin (314t) + 500 \sin (942t + 90^\circ)$ is applied to a series combination of a resistance 100Ω and an inductor of $0.5H$. Find the RMS value of $v(t)$, $i(t)$. Find the power delivered to the load and hence power factor. 8 M

5. a) Derive an expression for the decay current in an RC circuit excited by a unit step voltage. What is the time constant of the circuit? 8 M

b) For the circuit shown in Figure 5(b) find the expression for transient current when the switch is closed at $t = 0$. 8 M

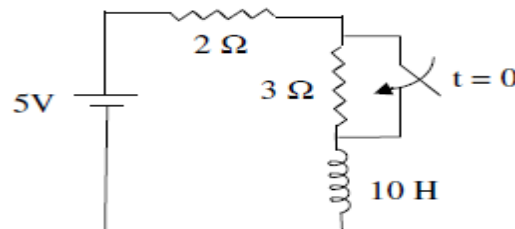


Figure 5(b)

6. a) A series RLC circuit, with $R = 5\Omega$, $L= 0.1H$, and $C = 500\mu F$, has a sinusoidal voltage source, $v(t)=1000 \sin 250t$. Derive the expression for current and the resulting current if the switch is closed at $t=0$. 8 M

b) A sinusoidal voltage of $12 \sin 8t$ volts is applied at $t=0$ to a series circuit of $R=4\Omega$ and $L =1H$. By Laplace transform method determine the circuit current $i(t)$ for $t \geq 0$. Assume zero initial conditions. 8 M