

Code: EE4T4

**II B.Tech - II Semester – Regular/Supplementary Examinations  
October 2020**

**ELECTRICAL MEASUREMENTS AND  
INSTRUMENTATION  
(ELECTRICAL & ELECTRONICS ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

**PART – A**

Answer *all* the questions. All questions carry equal marks

11 x 2 = 22 M

1.

- a) Distinguish LPF and UPF watt meters.
- b) What is the purpose of an instrument? And how are they classified.
- c) What is spring control and gravity control?
- d) Define Ratio Correction Factor.
- e) What is Potential Transformer?
- f) Write the working principle of Ratio Type Frequency Meter.
- g) Calculate the insulation resistance of a length of cable in which voltage falls from 120 to 80 Volts in 20 seconds, the capacitor being  $0.0004 \mu\text{F}$ .
- h) Define Quality Factor and how it is to be measured.
- i) What are the specifications of digital voltmeters?
- j) Differentiate between active and passive transducers.
- k) State the advantages of a DVM over an analog meter.

## PART – B

Answer any **THREE** questions. All questions carry equal marks.

3 x 16 = 48 M

2. a) Explain the working of Induction type single phase Energy meter with a neat diagram. 8 M
- b) Explain the different sources of errors in Induction type Energy meter and how they can be adjusted/compensated. 8 M
3. a) Derive the expressions for the ratio and phase angle errors of a current transformer with a neat phasor diagram. 8 M
- b) Calculate the i) flux in the core, ii) Ratio error at full load if the primary winding of a 1200/6A, 50 Hz current transformer has a single turn. Its secondary burden consists of a non – inductor impedance of  $1.6 \Omega$ . If the iron loss in the core is 1.6 W at full load and magnetizing mmf is 80 AT. Neglect leakage reactance. 8 M
4. a) Explain the working of Dynamometer type single phase power factor meter with a neat diagram. 8 M
- b) Explain working principle and operation of Electrical resonance type frequency meter with a neat diagram. 8 M

5. a) Deduce the equations when the bridge is balanced with a help of neat diagram of the Anderson Bridge. Draw the phasor diagram of the bridge. 8 M

b) Calculate the unknown R and C if a balanced 1 KHz bridge has the following configuration:

Arm AB:  $R_1 = 1000\Omega$  in parallel with  $C_1 = 0.053\mu\text{F}$

BC:  $R_2 = 1500\Omega$  in series with  $C_2 = 0.53\mu\text{F}$

CD: the unknown

DA: Pure capacitance  $C_4 = 0.265\mu\text{F}$ .

Draw the phasor diagram of the above bridge under balanced condition. 8 M

6. a) Explain briefly with neat diagrams the working of integrating type DVM. 8 M

b) Find the resolution of a  $3\frac{1}{2}$  digital voltmeter which is used for measuring voltage. How would a voltage of 14.42 be displaced on 10 V range? How would be a reading 14.42 be displaced on 100 V range? 8 M