

Code: EC4T3

**II B.Tech - II Semester – Regular/Supplementary Examinations –
April 2017**

**ANALOG ELECTRONIC CIRCUITS
(ELECTRONICS & COMMUNICATION ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

PART – A

Answer *all* the questions. All questions carry equal marks

11 x 2 = 22

1.

- a) Why h-parameters are suitable to model a transistor?
- b) Compare CC amplifier with CE amplifier.
- c) Draw the high frequency CE model of transistor.
- d) Explain the significance of gain bandwidth product.
- e) Draw the small signal model of a CS amplifier.
- f) Explain the need of cascading amplifiers.
- g) State Miller's and duality of Miller's theorem.
- h) Draw the practical circuit for voltage shunt feedback amplifier.
- i) What are the general characteristics of negative feedback amplifiers?
- j) List the advantages of crystal oscillator.
- k) What is crossover distortion and how it can be eliminated?

PART – B

Answer any **THREE** questions. All questions carry equal marks.

3 x 16 = 48 M

2. a) Compare the characteristics of transistor amplifiers in the three configurations. 6 M

b) Consider a single stage CE amplifier with $R_s=1K\Omega$, $R_1=50K\Omega$, $R_2=2K\Omega$, $R_c=2K\Omega$, $R_L=2K\Omega$, $h_{fe}=50$, $h_{ie}=1.1K$, $h_{oe}=25\mu A/V$ and $h_{re}=2.5 \times 10^{-4}$ as shown in figure 1. Find A_i , R_i , A_v , A_{v_s} and R_o . Assume that C_1 , C_2 and C_e are large at the operating frequency range.

10 M

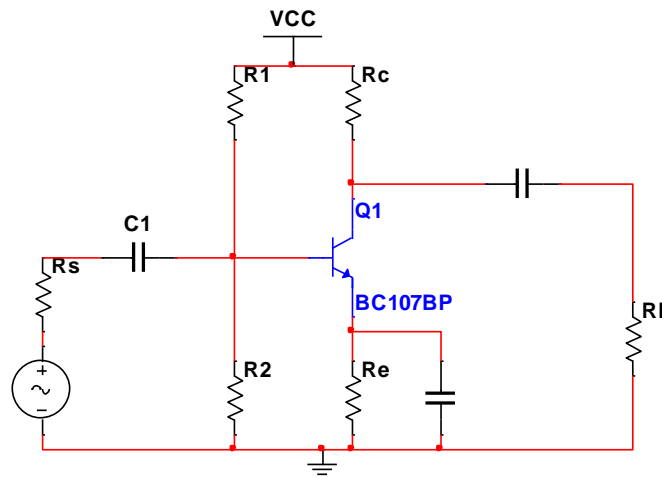


Figure 1

3. A transistor 's short circuit current gain is measured to be 25 at a frequency of 2 MHz. If the transistor's $f_\beta=200$ kHz Determine :

a) The current gain bandwidth product, f_T 5 M

b) The transistor h_{fe} at low frequency. 5 M

- c) The short circuit current gain at 10 MHz and 100 MHz. 6 M
4. a) Explain different coupling schemes used in multistage amplifiers with their frequency response. 8 M
- b) Derive the expressions for A_i , R_i , A_v and R_o of bootstrapped Darlington pair. 8 M
5. a) For the voltage series feedback amplifier, derive the expression for gain, input resistance and output resistance. 10 M
- b) Calculate the gain, input impedance, output impedance of voltage series feedback amplifier having $A=-300$, $R_i=1.5K$, $R_o=50K$ and $\beta=-1/20$. 6 M
6. a) Draw and Explain the working of Hartley oscillator. 8 M
- b) Explain transformer coupled class A amplifier and find its efficiency. 8 M