

Code: EC4T3

**II B.Tech - II Semester – Regular Examinations – May 2016**

**ANALOG ELECTRONIC CIRCUITS  
(ELECTRONICS AND COMMUNICATION ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

**PART – A**

Answer *all* the questions. All questions carry equal marks

11x 2 = 22 M

1.

- a) Which configuration (CE, CB, CC) is preferred to design a power amplifier? Justify your answer.
- b) Suggest an appropriate transistor amplifier for (i) High Voltage gain (ii) High current gain.
- c) What is the phase shift for (i) two stage CE amplifier (ii) two stage CB amplifier.
- d) Define  $\beta$ , cutoff frequency and  $f_T$ .
- e) At room temperature BJT in CE configuration is operating at  $I_C = 2mA$  and  $V_{CE} = 10V$ . Calculate its transconductance.
- f) Draw the small signal model of JFET in CS configuration.
- g) Draw the frequency response of RC coupled amplifier and direct coupled amplifier.

- h) Is CE amplifier with emitter resistance circuit acts as a feedback amplifier? If yes, which type of feedback amplifier it is.
- i) Consider an amplifier with gain 20 and bandwidth 10KHz. If positive feedback is provided with a feedback factor of 0.1 what is the new bandwidth?
- j) Suggest an appropriate Oscillator for (i) High frequency applications (ii) Low frequency applications
- k) Is power amplifier amplifies the power directly? Justify your answer.

## PART – B


Answer any **THREE** questions. All questions carry equal marks.

$$3 \times 16 = 48 \text{ M}$$

2.

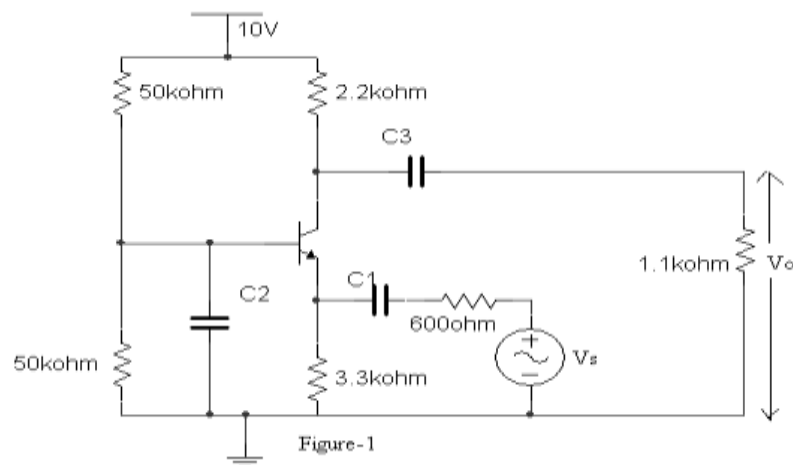- a. Calculate current gain, overall voltage gain, input and output resistances for the amplifier shown in figure-1. Here for the transistor

$$h_{rb} = 0, h_{ib} = 25\Omega, h_{fb} = -0.99, h_{ob} = 1 \mu\text{S}. 10 \text{ M}$$



b. Derive an expression for voltage gain of CE amplifier with emitter resistance. 6 M

3.


a. Draw the equivalent circuit of a transistor at high frequencies and derive an expression for feedback conductance, input conductance and base spreading resistance. 8 M

b. Derive an expression for CE short circuit current gain at high frequencies. 8 M

4.

a. Calculate voltage gain and input impedance for the circuit shown in figure-2. Here for FET, transconductance is  $6\text{m}\Omega$  and drain resistance is  $5\text{K}\Omega$ .

8 M

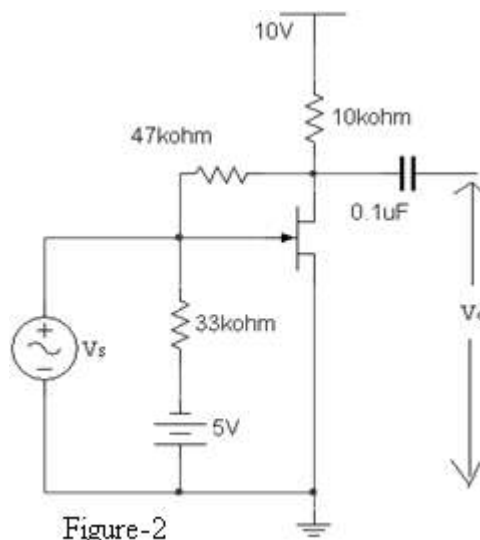

- b. Derive an expression for lower and upper cutoff frequencies of multistage amplifier in terms of single stage amplifier. 8 M
- 5.
- a. Derive an expression for input and output resistance of current shunt feedback amplifier. 8 M
- b. A single stage CE amplifier has a Voltage gain of 800 without feedback. When feedback is employed, its gain reduces to 70. Calculate the percentage of the output which is fed back to the input. 8 M
- 6.
- a. Explain the working of Wien Bridge Oscillator using BJT. Also derive the expression for the frequency of Oscillation. 8 M
- b. Explain the operation of complementary symmetry push pull amplifier. 8 M