

Code: EC5T1

III B.Tech - I Semester–Regular Examinations December 2016

**LINEAR INTEGRATED CIRCUITS
(ELECTRONICS AND COMMUNICATION ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

PART – A

Answer *all* the questions. All questions carry equal marks

11x 2 = 22 M

1.

- a) What is the need of level translator in Op-Amp?
- b) Draw the equivalent circuit of OP-Amp indicating the parameters.
- c) Define the output offset voltage and input bias current.
- d) Draw the circuit diagram of Op-Amp buffer.
- e) List out the differences between Wien bridge and RC phase shift oscillator.
- f) What are the applications of All pass filters?
- g) Draw the circuit diagram of Butterworth Low pass filter of first order.
- h) What voltage should be applied and to which pin to reset the 555 Timer?
- i) Define the Capture range and Lock range of PLL.
- j) Define Resolution and Accuracy of D to A converter.
- k) Which is the fastest A to D converter and why?

PART – B

Answer any **THREE** questions. All questions carry equal marks.

$$3 \times 16 = 48 \text{ M}$$

2. a) Analyse the Dual input balanced output differential amplifier and derive the equation for differential mode gain using h-parameter model. 10 M
- b) Discuss about the measurement of Slew rate. 6 M
3. a) Explain the operation of Instrumentation amplifier with the help of block diagram and derive equation for gain . 8 M
- b) Design a Wien bridge oscillator with gain of 5 and 1 KHz frequency. 8 M
4. a) Construct a first order butter worth wide band pass filter with pass band gain of 4 to pass a band of 3KHz-5KHz. 8 M
- b) Explain the principle of switched capacitor filters and their advantages. 8 M
5. a) Explain the Frequency divider using 555 Timer. 8 M
- b) Explain the Frequency demodulation using 565 PLL. 8 M

6. a) Discuss about the working of R-2R Ladder D-to-A Converter. 8 M
- b) Explain the operation of Successive approximation A-to-D Converter. 8 M