

Code: EE5T6

III B.Tech - I Semester – Regular Examinations - December 2016

**LINEAR AND DIGITAL INTEGRATED CIRCUIT
APPLICATIONS
(ELECTRICAL & ELECTRONICS ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

PART – A

Answer *all* the questions. All questions carry equal marks

11 x 2 = 22 M

1.

- a) Explain why the open-loop op-amp configurations are not used in linear applications?
- b) What is the output voltage and approximate output current of an op-amp when the load resistor of an op-amp is short circuited?
- c) Justify the statement that op-amp is a Voltage Controlled Voltage source.
- d) List the advantages and disadvantages of Switched Capacitor filter.
- e) What is frequency stability in oscillator and give its significance?
- f) List the features of 555 timer.
- g) List the basic building blocks of the discrete Phased Locked Loop.
- h) Draw the logic diagram of 74x138 3-to-8 decoder.
- i) Write a design procedure of combinational circuits.


- j) List the applications of Flip-flops.
 k) Write the specifications of shift register IC's.

PART – B

Answer any *THREE* questions. All questions carry equal marks. 3 x 16 = 48 M

2. a) Define the following op-amp parameters 8 M
i) Differential input resistance *ii)* input offset voltage
iii) offset voltage adjustment range *iv)* Slew rate

 - b) Find V_{out} & I_{out} for the circuit shown below. 8 M



3. a) Explain the operation of RC phase shift oscillator with neat sketch. 8 M

- b) Assuming suitable data design for a first order low pass filter at cut-off frequency of 1KHz with a pass band gain of 2. 8 M

4. a) Design a Monostable Multivibrator using 555 timer to produce a pulse width of 100 msec. 8 M
- b) Give the functional block diagram of VCO NE566 and explain its working and derive the necessary expression for free running frequency. 8 M
5. a) Design a 4 to 16 decoder using two 74x138 decoders. 8 M
- b) Design a parallel binary adder. 8 M
6. a) Draw the logic diagram of 74x194 shift register and explain the operation. 8 M
- b) Design a circuit to convert a T-flipflop to J-K flipflop. 8 M