

Code: 19EE4501B

III B.Tech - I Semester – Regular Examinations – JANUARY 2022**ELECTRICAL MEASUREMENTS
(ELECTRICAL & ELECTRONICS ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

-
- Note: 1. This question paper contains two Parts A and B.
2. Part-A contains 5 short answer questions. Each Question carries 2 Marks.
3. Part-B contains 5 essay questions with an internal choice from each unit. Each question carries 12 marks.
4. All parts of Question paper must be answered in one place
-

PART – A

1. a) Define recording and integrating instruments with one example.
- b) State two applications of CT and PT.
- c) What is the purpose of compensating coil in wattmeter?
- d) Write the advantages of Maxwell's bridge?
- e) What are the properties of a passive transducer?

PART – B**UNIT – I**

2. a) Explain how the ranges of ammeters and voltmeters can be extended? 6 M
- b) Design an Aryton shunt to provide an ammeter with the current ranges 1 A, 5 A and 10 A. A basic meter resistance is 50Ω and full scale deflection current is 1 mA? 6 M

OR

3. a) Explain the purpose of lag adjustment devices in an Induction type of energy meter. Explain the different ways of achieving it? 6 M
- b) List the advantages & disadvantages of MI type instruments. 6 M

UNIT – II

4. a) Why secondary of C.T should not be open? 4 M
- b) A current transformer with single turn primary has 300 secondary turns and $R = 1.5$, iron loss of 1.2W and $X = 1\Omega$. When secondary carries 5 A current, magnetising m.m.f at of 100 A and calculate ratio and phase angle errors. 8 M

OR

5. a) With neat figure explain the working of Potential Transformer. 6 M
- b) A potential transformer of ratio 1000/100 has primary resistance 94.5Ω , secondary resistance 0.86Ω , primary reactance 66.2Ω , total equivalent reactance 110Ω , and no load current 0.02A at 0.4 power factor. Calculate the phase angle error at no load. 6 M

UNIT-III

6. a) Explain the construction and working of moving iron type power factor meters with neat diagram. 8 M
- b) Explain the advantages and disadvantages of moving iron type power factor meters. 4 M

OR

7. a) What are the different methods of measurement of frequency in the power frequency range. 4 M

- b) Explain the working of Weston Type Frequency meter with neat diagram. 8 M

UNIT – IV

8. a) Explain how the inductance is measured in terms of known capacitance using Maxwell's bridge? 6 M
- b) Explain the kelvins double bridge method for the measurement of low resistance with a neat diagram. 6 M

OR

9. a) A Maxwell bridge is used to measure inductive impedance. The bridge consists at balance are $R_1 = 47 \text{ k}\Omega$ and $C_1 = 0.01 \text{ }\mu\text{F}$ in arm AB, $R_2 = 5.1 \text{ k}\Omega$ in arm BC, $R_3 = 100 \text{ k}\Omega$ in arm AD. Find the unknown impedance? 8 M
- b) Explain how an unknown resistance can be measured by Wheatstone bridge. 4 M

UNIT – V

10. a) Explain in detail about the factors to be considered while selecting a transducer. 6 M
- b) Discuss in detail about the advantages and limitations of Thermistor. 6 M

OR

11. a) Describe with neat sketch, the working of digital phase angle meter. 6 M
- b) Explain with neat diagram the operation of a DVM. State the advantages of DVM. 6 M