

Code: EE5T5

III B.Tech - I Semester – Regular Examinations - November 2014

**LINEAR & DIGITAL INTEGRATED CIRCUIT
APPLICATIONS
(ELECTRICAL & ELECTRONICS ENGINEERING)**

Duration: 3 hours

Marks: 5x14=70

Answer any FIVE questions. All questions carry equal marks

1. a) List out AC characteristics of an op-amp and discuss about them? 7 M

- b) An op-amp has a slew rate of $2V/\mu s$. What is the maximum frequency of an output sinusoid of peak value 5V at which the distortion sets in due to the slew rate limitation? Derive the formula used? 7 M

2. a) Explain and draw the output waveforms of an ideal integrator circuit when the input is square wave? 7 M

- b) Design a circuit using op-amp to generate a output $V_0=0.1V_1 - V_2 + 10V_3$ where V_1, V_2, V_3 are input voltages. 7 M

3. a) Describe the operation of logarithmic amplifier using OP-AMP? 7 M

- b) List the conditions for oscillations in all the three types of oscillators namely RC Phase, shift, Wien bridge and Quadrature Oscillators? 7 M

4. a) Configure a 555 timer as a Schmitt trigger and explain? 7 M
- b) Explain about the free running range, capture range and lock range in PLL with necessary equations? 7 M
5. a) Design a narrow band pass filter using Op-Amp. The resonant frequency is 100Hz and $Q=2$. Assume $C=0.1\mu\text{F}$. 7 M
- b) Draw the schematic diagram of successive approximation type analog to digital converter and explain the operation? 7 M
6. a) Describe the terms decoder and demultiplexer. How can you convert a decoder to demultiplexer? 7 M
- b) Draw and explain the working of ripple adder? 7 M
7. a) Explain the operation of 4 bit Johnson counter? 7 M
- b) Specify the modes of operation of shift registers? 7 M
8. a) Differentiate between static RAM and dynamic RAM? 7 M
- b) Write about any two programmable logic devices? 7 M