

Code: EC5T1

**III B.Tech - I Semester – Regular/Supplementary Examinations
October 2017**

**LINEAR INTEGRATED CIRCUITS
(ELECTRONICS AND COMMUNICATION ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

PART – A

Answer *all* the questions. All questions carry equal marks

11x 2 = 22 M

1.

- a) Draw the block diagram of an ideal op-amp.
- b) Define CMRR for a differential amplifier.
- c) With the help of circuit diagram find the gain of an inverting amplifier.
- d) Draw the circuit diagram of log amplifier.
- e) Mention any two advantages of active filters.
- f) Mention any two applications of All-pass filter.
- g) Mention any two applications of 555 timer in Astable-mode of operation.
- h) Draw the pin diagram of 555 timer.
- i) Mention any two applications of 565 PLL.
- j) Mention any two advantages of R-2R ladder DAC over weighted resistor DAC over.
- k) What is the principle of D/A converter?

PART – B

Answer any **THREE** questions. All questions carry equal marks.

$$3 \times 16 = 48 \text{ M}$$

2.a) With the help of circuit diagram derive the expression for differential voltage gain for a differential amplifier. 8 M

b) Explain the following with respect to the operational amplifier: 8 M

i) Slew rate

ii) Input Offset current

iii) Input Offset Voltage

iv) Common mode rejection ratio

3.a) i) Design an Inverting operation amplifier which has the closed loop voltage gain of $A_F = -80$. The input voltage is $V_S = 200 \text{ mV}$ with a source resistance of $R_S = 500 \Omega$. Find the value of output voltage V_O . The DC supply voltages are $V_{CC} = V_{EE} = 12 \text{ V}$. 4 M

ii) List any 4 characteristics of an Ideal operational amplifier. 4 M

b) i) With the help of a circuit diagram explain the functioning of anti-log amplifiers. 4 M

ii) With the help of a circuit diagram explain the functioning of square wave generator. 4 M

- 4.a) Design a first order high-pass filter to give a high cutoff frequency of $f_o = 5 \text{ KHz}$ with a pass band gain of 10. 8 M
- b) With the help of a neat circuit diagram explain the working of Band-pass filters. 8 M
- 5.a) With the help of neat sketches explain the functioning of Astable multi-vibrator using 555 timer. 8 M
- b) With the help of neat circuit diagram explain the functioning of 565 PLL in detail. 8 M
- 6.a) Explain briefly about the Counter type ADC. 8 M
- b) With the help of neat circuit diagram explain the functioning of weighted resistor DAC. 8 M