

Code: EE6T5

III B.Tech-II Semester–Regular/Supplementary Examinations–March 2019

**POWER SYSTEM ANALYSIS
(ELECTRICAL & ELECTRONICS ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

PART – A

Answer *all* the questions. All questions carry equal marks

11x 2 = 22 M

1. a) Define symmetrical short circuit current.
- b) Write formula for converting PU values from one base to other base values.
- c) Define short circuit MVA.
- d) What is the need for short circuit analysis?
- e) Define negative sequence impedance.
- f) What is the necessity of power flow studies.
- g) Explain why direct solution of load flow problem is not possible.
- h) Write the advantages of N-R method.
- i) What is Jacobian matrix?
- j) Define ‘stability’ of power system?
- k) Define transient stability.

PART – B


Answer any *THREE* questions. All questions carry equal marks.

$$3 \times 16 = 48 \text{ M}$$

2. a) What are the advantages of per-unit computations? 6 M
- b) A three phase transmission line operating at 33kV and having a resistance of 5ohms and reactance of 20ohm is connected to generating station through 11kV/33kV 15MVA step-up, 5% reactance transformer connected to the bus bar are two alternators one of 11kV, 10MVA with 10% reactance and another of 11kV, 5 MVA with 7.5% reactance. Calculate the short circuit MVA fed to the symmetrical fault between phases if it occurs at the end of the transmission line. 10 M
3. a) The line to ground voltages on high voltage side of step up transformer are 100 kV, 33 kV and 38 kV on phases a, b & c respectively . The voltages of phase 'a' lead that of phase 'b' by 100° and lag that of phase 'c' by 176.5° . Determine analytically the symmetrical components of voltages. 8 M
- b) Derive an expression for fault current when double line to ground fault occurs on the terminals of a unloaded alternator? Draw the sequence network diagram. 8 M
4. a) Explain with suitable example, formulation of Y_{bus} by direct inspection method. 6 M

- b) A two bus system is shown in below figure. Calculate the bus 2 voltage at the end of first iteration by G-S method. The elements of bus admittance matrix are $Y_{11} = Y_{22} = 1.5 \angle -86^\circ$ P.U and $Y_{21} = Y_{12} = 1.8 \angle -110^\circ$ P.U.

10 M

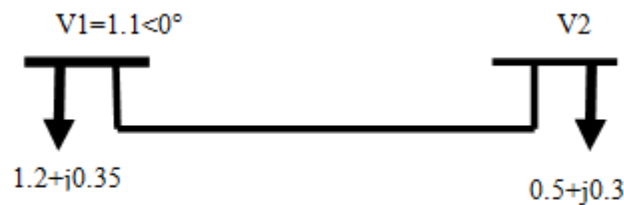

5. a) Consider the single line diagram of a power system shown in figure. Take bus 1 as slack bus and Y_{bus} matrix is given below:


12 M

$$Y_{bus} = \begin{bmatrix} 3 - j5 & -1.2 + j6 & -1.5 + j8 \\ -1.2 + j6 & 4 - j12 & -3 + j6 \\ -1.5 + j8 & -3 + j6 & 5 - j6 \end{bmatrix}$$

Schedule of generation and loads are as follows

Bus No.	Generation		Load		Assumed Bus voltages
	MW	MVAR	MW	MVAR	
1	0	0	0	0	$1.04 + j0.0$
2	0	0	250	150	$1.0 + j0.0$
3	100	70	50	20	$1.0 + j0.0$

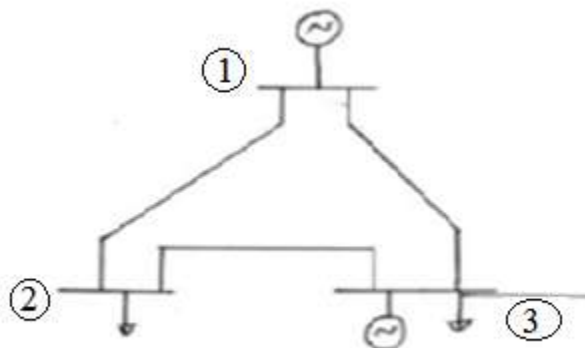Using Newton-Raphson method, obtain bus voltages at the end of 1st iteration.



b) Compare Newton-Raphson and Fast Decoupled Load Flow methods. 4 M

6. a) What is Equal area Criterion? Discuss the application of Equal area criterion for the System Stability when a sudden change in mechanical input. 8 M

b) Define and briefly explain the terms with respect to stability 8 M

i) Steady state stability power limit.

ii) Transfer Reactance.

iii) Synchronizing power coefficient.