

Code: EE6T4

III B.Tech - II Semester – Regular/Supplementary Examinations March 2020

POWER SEMICONDUCTOR DRIVES
(ELECTRICAL & ELECTRONICS ENGINEERING)

Duration: 3 hours

Max. Marks: 70

PART – A

Answer *all* the questions. All questions carry equal marks

11x 2 = 22 M

1.

- a) What are the advantages of electrical drives?
- b) What are the components of load torque?
- c) Write the fundamental torque equation.
- d) What are the advantages of three phase drives over single phase drives?
- e) List method used for multi-quadrant operation of separately excited DC motor fed from fully controlled rectifier.
- f) Under what condition regenerative braking may employ to DC series motor?
- g) List out the advantages offered by DC chopper drives over line commutated converter controlled DC drives.
- h) Compare of VSI and CSI drives.
- i) Draw the circuit diagram for speed control of induction motor by stator voltage control.
- j) Write the equation to transform from three phases to two phases.
- k) What is vector control of an induction motor?

PART – B

Answer any *THREE* questions. All questions carry equal marks.

3 x 16 = 48 M

2. a) Draw the block diagram of basic electrical drive system.
Explain each component. 10 M
- b) What are the main factors which decide the choice of electrical drive for a given application? 6 M
3. a) Explain the operation of a separately excited DC motor supplied from 3- Φ fully controlled rectifier with necessary diagrams. Assume Continuous conduction. 8 M
- b) A 200 V, 875 rpm, 150 A separately excited DC motor has an armature resistance of 0.06 Ω . It is fed from a single phase full converter with an AC source voltage of 220 V, 50 Hz. Assume continuous load current,
- (i) Calculate firing angle for rated motor torque and 750 rpm
- (ii) Calculate firing angle for rated motor torque and -750 rpm
- (iii) Calculate motor speed for firing angle 160° and rated motor torque. 8 M

4. a) Describe the first quadrant chopper control of separately excited DC motor. 8 M
- b) Explain the operation of a separately excited DC motor supplied from 1- Φ Dual converter with necessary diagrams. 8 M
5. a) Draw the circuit diagram and explain the working of a slip power recovery system using static Scherbius system for a three phase induction motor. 10 M
- b) Draw and explain principle of operation of cascaded H-bridge 5 level inverter fed induction motor. 6 M
6. a) Deduce Park's transformations for 3- Φ to d-q axes system. 8 M
- b) Explain about DTC control of induction motor. 8 M