

Code: EE7T4

**IV B.Tech - I Semester – Regular/Supplementary Examinations
October - 2019**

**FLEXIBLE AC TRANSMISSION SYSTEMS
(ELECTRICAL & ELECTRONICS ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

PART – A

Answer *all* the questions. All questions carry equal marks

11 x 2 = 22 M

1.

- a) Analyze the IEEE definition of FACTS controller.
- b) List the different stability issues that limits the transmission capability.
- c) Analyze the importance of power flow controllable parameters.
- d) Illustrate the basic circuit of current source converter.
- e) Draw single phase-leg circuit of converter.
- f) Illustrate the circuit diagram of midpoint voltage regulation for line segmentation.
- g) Summarize the expression for active power with shunt compensator.
- h) Draw the block diagram for the transient stability enhancement with SVC & STATCOM.
- i) Illustrate the block diagram for the power oscillation damping with SVC & STATCOM.

- j) Summarize the expression for reactive power with series compensator.
- k) Draw the basic circuit representation of IPFC.

PART – B

Answer any **THREE** questions. All questions carry equal marks.

$$3 \times 16 = 48 \text{ M}$$

- 2. a) Explain the basic types of FACTS controllers with neat diagrams. 8 M
- b) Discuss the benefits of FACTS controllers. 8 M
- 3. a) Explain the single phase full wave bridge converter with neat diagrams. 8 M
- b) Compare the current source converter with voltage source converter. 8 M
- 4. a) Explain the objectives of shunt compensation in transmission lines. 8 M
- b) Demonstrate the operation of the Thyristor Switched Reactor with neat diagram. 8 M

5. a) Demonstrate the operating point control scheme for static VAR compensators. 8 M
- b) Explain the summary of compensation control with necessary block diagrams. 8 M
6. a) Explain the operation of Thyristor Controlled Series Capacitor with neat diagram. 8 M
- b) Discuss the control schemes for Thyristor Switched Series Capacitor. 8 M