

Code: EE7T4

IV B.Tech - I Semester – Regular Examinations – October - 2017

**FLEXIBLE AC TRANSMISSION SYSTEMS
(ELECTRICAL & ELECTRONICS ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

PART – A

Answer *all* the questions. All questions carry equal marks

11 x 2 = 22

1.

- a) What are FACTS controllers? What are their benefits?
- b) How would you explain the objective of reactive shunt compensation in transmission lines?
- c) How would you compare VSC and CSC?
- d) How would you explain the Power Oscillations can be damped out by both series and shunt compensation?
- e) How would you describe IPFC?
- f) How would you explain the necessity of shunt compensation from the view point of mid point voltage regulation?
- g) What is SVC? What are its applications?
- h) How do you compare the STATCOM and SVC in terms of their operation?
- i) What are the problems with interconnected power systems?

- j) How would you discuss the types of converters basically used in FACTS devices & what are the differences between them?
- k) Why transient free switching of TSC is needed?

PART – B

Answer any **THREE** questions. All questions carry equal marks.
3 x 16 = 48 M

2. a) How would you explain the power flow and dynamic stability considerations in the Interconnected power systems. And also list out relative importance of Controllable parameters. 8 M
- b) Why transmission interconnections are necessary and what are the major constraints of today's power system? 8 M
3. a) How would you explain the Three level Voltage Source Converter with neat diagrams? 8 M
- b) How would you explain the types of harmonics are present in the output of 3 phase bridge converter? 8 M
4. a) How would you describe the transient stability can be improved by shunt compensation? 8 M

- b) How would you explain the operation of TSC with neat diagrams? 8 M
5. a) How would you describe the performance of VSC based STATCOM? 8 M
- b) How would you explain about the role of SVC in improving the stability limit and enhancing the power system damping? 8 M
6. a) How would you explain the concept of series capacitive compensation? 8 M
- b) How would you describe series compensation can be used for power oscillation damping? 8 M